

# Quiz 1

(September 12th @ 9:30 am)

## PROBLEM 1 (20 PTS)

Complete the truth table for a circuit that activates an output ( $f = '1'$ ) when the decimal value of the 3 input bits is equal to 1, 4, or 5. Then, simplify the function using Karnaugh maps.

| x | y | z | f     |
|---|---|---|-------|
| 0 | 0 | 0 | $m_0$ |
| 0 | 0 | 1 | $m_1$ |
| 0 | 1 | 0 | $m_2$ |
| 0 | 1 | 1 | $m_3$ |
| 1 | 0 | 0 | $m_4$ |
| 1 | 0 | 1 | $m_5$ |
| 1 | 1 | 0 | $m_6$ |
| 1 | 1 | 1 | $m_7$ |

| xy | 00    | 01    | 11    | 10    |
|----|-------|-------|-------|-------|
| 0  | $m_0$ | $m_2$ | $m_6$ | $m_4$ |
| 1  | $m_1$ | $m_3$ | $m_7$ | $m_5$ |

| x | y | z | f |
|---|---|---|---|
| 0 | 0 | 0 |   |
| 0 | 0 | 1 |   |
| 0 | 1 | 0 |   |
| 0 | 1 | 1 |   |
| 1 | 0 | 0 |   |
| 1 | 0 | 1 |   |
| 1 | 1 | 0 |   |
| 1 | 1 | 1 |   |

| xy | 00 | 01 | 11 | 10 |
|----|----|----|----|----|
| 0  |    |    |    |    |
| 1  |    |    |    |    |

$f =$

## PROBLEM 2 (30 PTS)


Complete the timing diagram of the logic circuit whose VHDL description is shown below:

```

library ieee;
use ieee.std_logic_1164.all;


entity circ is
  port ( a, b, c: in std_logic;
        f: out std_logic);
end circ;

 architecture st of circ is
  signal x: std_logic;
begin
  x <= a and b;
  f <= x xnor c;
end st;
    
```


 
## PROBLEM 3 (20 PTS)

Design a circuit that verifies the logical operation of a NOT gate.  $f = '1'$  (LED ON) if the NOT gate works improperly. Assumption: when the NOT gate is not working, it generates 1's instead of 0's and vice versa.



## PROBLEM 4 (30 PTS)

- Convert the following decimal number to i) binary, and ii) hexadecimal. You MUST show your procedure.
  - 113.6875
- A microprocessor is able to handle memory addresses from 0x0000 to 0x3FFF. How many bits do we need to represent those addresses?