


# Solutions - Final Exam

(December 10th @ 7:30 am)

Clarity is very important! Show your procedure!

 
## PROBLEM 1 (12 PTS)

- Complete the timing diagram of the following circuit.  $Q = Q_3Q_2Q_1Q_0$



PROBLEM 2 (10 PTS)

- We want to design a counter modulo-6 (count from 0 to 5) with enable using a State Machine. The counter must assert an output  $z = '1'$  when the count reaches 5.
- Provide the State Diagram (any representation) and the Excitation table  $||Inputs|Present State||Next State|Outputs||$ . Is this a Moore or a Mealy machine?

 


E	PRESENT STATE		z	PRESENT STATE				NEXTSTATE						
	E	STATE		STATE	z	E	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	(t)	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	(t+1)
0	S1	S1	0	0	0	0	0	0	0	0	0	0	0	0
0	S2	S2	0	0	0	0	1	0	0	0	1	0	0	0
0	S3	S3	0	0	0	1	0	0	0	1	0	0	0	0
0	S4	S4	0	0	0	1	1	0	0	1	1	0	0	0
0	S5	S5	0	0	1	0	0	0	1	0	0	0	0	0
0	S6	S6	1	0	1	0	1	0	1	0	1	0	1	1
1	S1	S2	0	0	1	1	0	0	X	X	X	X	X	X
1	S2	S3	0	0	1	1	1	0	X	X	X	X	X	X
1	S3	S4	0	1	0	0	0	0	0	0	1	0	0	0
1	S4	S5	0	1	0	0	1	0	0	1	0	0	0	0
1	S5	S6	0	1	0	1	1	0	1	0	1	0	0	0
1	S6	S1	1	1	0	1	0	0	1	0	1	0	0	0
1	S1	S2	0	1	1	0	1	0	0	0	0	0	1	1
1	S2	S3	0	1	1	1	0	1	X	X	X	X	X	X
1	S3	S4	0	1	1	1	1	0	X	X	X	X	X	X
1	S4	S5	0	1	1	1	1	1	X	X	X	X	X	X
1	S5	S6	0	1	1	1	1	1	X	X	X	X	X	X
1	S6	S1	1	1	1	1	1	1	X	X	X	X	X	X


**MOORE MACHINE**

 PROBLEM 3 (15 PTS)

- Given the following system, complete the Timing Diagram.
- The LUT 6-to-6 implements the following function:  $OLUT = \lceil \sqrt{ILUT} \rceil$



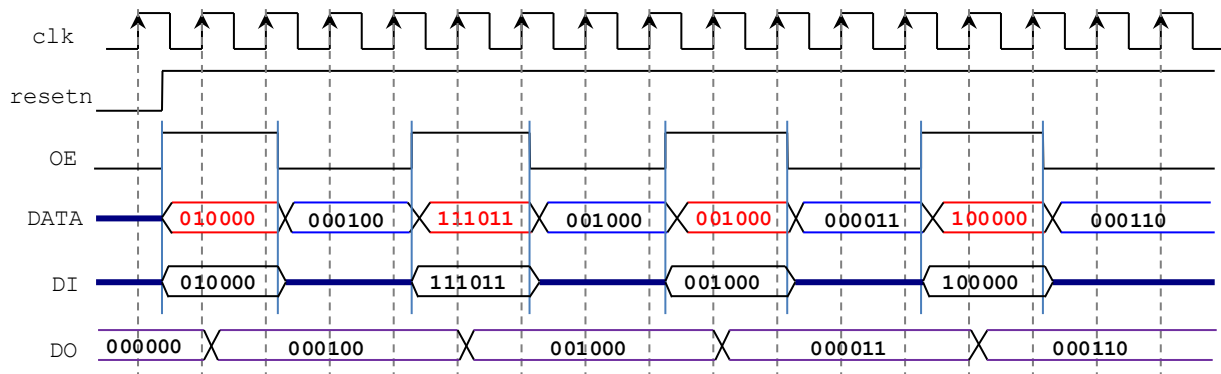$\lceil \sqrt{16} \rceil = 4$   
 $\lceil \sqrt{59} \rceil = 8$   
 $\lceil \sqrt{8} \rceil = 3$   
 $\lceil \sqrt{32} \rceil = 6$




PROBLEM 4 (18 PTS)

- Provide the State Diagram (any representation) of the FSM whose VHDL description is shown below.
- Complete the Timing Diagram.


```
library ieee;
use ieee.std_logic_1164.all;

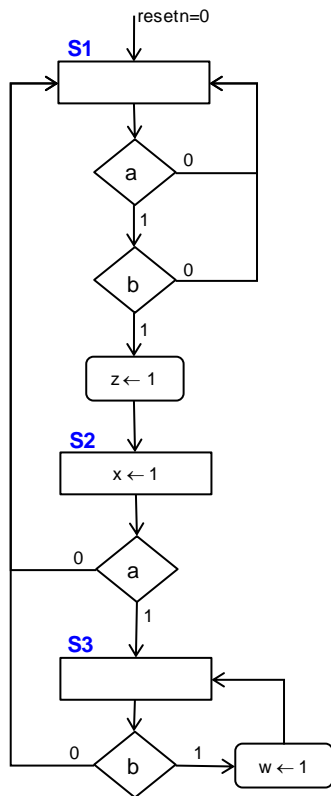entity circ is
port ( clk, resetn: in std_logic;
      a, b: in std_logic;
      x,w,z: out std_logic);
end circ;
```




```
architecture behavioral of circ is
type state is (S1, S2, S3);
signal y: state;
begin
Transitions: process (resetn, clk, a, b)
begin
if resetn = '0' then y <= S1;
elsif (clk'event and clk = '1') then
case y is
when S1 =>
if a = '1' then
if b = '1' then y <= S2;
else y <= S1; end if;
else
y <= S1;
end if;
when S2 =>
if a = '1' then y <= S3;
else y <= S1; end if;
when S3 =>
if b = '1' then y <= S1;
else y <= S3; end if;
end case;
end if;
end process;

 Outputs: process (y,a,b)
begin
x <= '0'; w <= '0'; z <= '0';
case y is
when S1 =>
if a = '1' and b = '1' then
z <= '1'; end if;
when S2 => x <= '1';
when S3 =>
if b = '1' then w <= '1'; end if;
end case;
end process;
end behavioral;
```



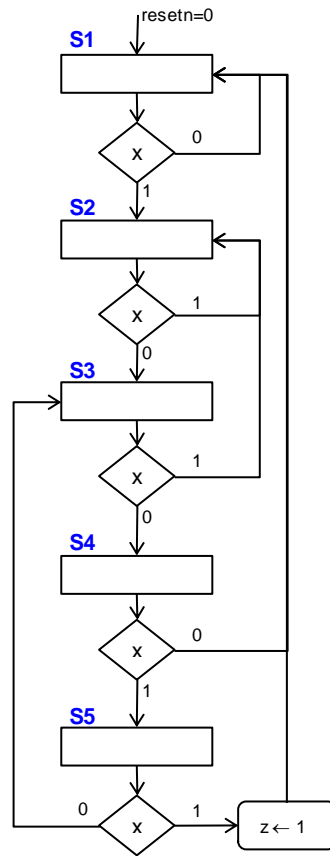PROBLEM 5 (10 PTS)

- Sequence detector (with overlap): Draw the state diagram (in ASM form) of a circuit (with an input 'x') that detects the following sequence: 10011. The detector must assert and output  $z = '1'$  when the sequence is detected.




PROBLEM 6 (15 PTS)

Basic Processor:

Available Registers: R0 (register 0, 4 bits), R1 (register 1, 4 bits), PC (program counter, 4 bits),  
OUT (output register, 4 bits)  
IR (instruction register, 8 bits)

Instruction Memory: Stores up to 16 8-bit instructions.

 Instruction Set: Instructions are specified on the Instruction Register (IR):



DR=0 ⇒ R0 is the destination register, DR=1 ⇒ R1 is the destination register.

SR=0 ⇒ R0 is the source register, SR=1 ⇒ R1 is the source register.

OPCODE (IR[7..5])	Instruction	Operation
000	MOV DR, SR	DR ← SR
001	LOADI DR, DATA	DR ← DATA, DATA = IR[3..0]
010	ADD DR, SR	DR ← DR + SR
011	ADDI DR, DATA	DR ← DR + DATA, DATA = IR[3..0]
100	SR0 DR, SR	DR ← 0&SR[3..1]
101	IN DR	DR ← IN
110	OUT DR	OUT ← DR
111	JNZ DR, ADDRESS	PC ← PC + 1 if DR=0 PC ← IR[3..0] if DR≠0 * ADDRESS = IR[3..0]

- Write an assembly program for a counter from 2 to 13: 2, 3, ..., 13, 2, 3, ... The count must be shown on the output register (OUT). Use labels to specify any address where your program jumps. Note that you can have only up to 16 instructions.
- Provide the contents of the Instruction Memory.

address	INSTRUCTION MEMORY
0000	00100010
0001	00110100
0010	11000000
0011	01100001
0100	01110001
0101	11110000
0110	00100001
0111	11100010
1000	
1001	
1010	
1011	
1100	
1101	
1110	
1111	

```

start: loadi R0,2
      loadi R1,4
loop:  out R0 → OUT: shows the count
      addi R0,1
      addi R1,1
      jnz R1, loop
      loadi R0,1
      jnz R0, start
    
```

