

n = 9 bits

$$\begin{array}{r} c_9=1 \\ c_8=0 \\ -255 = 100000001 + \\ -230 = 100011010 \\ \hline 000011011 \end{array}$$

overflow = $c_9 \oplus c_8 = 1 \rightarrow$ overflow!
 $-255 - 230 = -485 \notin [-2^8, 2^8 - 1] \rightarrow$ overflow!

To avoid overflow:

n = 10 bits (sign-extension):

$$\begin{array}{r} c_{10}=1 \\ c_9=1 \\ -255 = 1100000001 + \\ -230 = 1100011010 \\ \hline -485 = 1000011011 \end{array}$$

overflow = $c_{10} \oplus c_9 = 0 \rightarrow$ no overflow
 $-485 \in [-2^9, 2^9 - 1] \rightarrow$ no overflow

n = 10 bits

$$\begin{array}{r} c_{10}=0 \\ c_9=1 \\ +490 = 0111101010 + \\ +47 = 0000101111 \\ \hline 1000011001 \end{array}$$

overflow = $c_{10} \oplus c_9 = 1 \rightarrow$ overflow!
 $490 + 47 = 537 \notin [-2^9, 2^9 - 1] \rightarrow$ overflow!

To avoid overflow:

n = 11 bits (sign-extension):

$$\begin{array}{r} c_{11}=0 \\ c_{10}=0 \\ +490 = 00111101010 + \\ +47 = 00000101111 \\ \hline +537 = 01000011001 \end{array}$$

overflow = $c_{11} \oplus c_{10} = 0 \rightarrow$ no overflow
 $+537 \in [-2^{10}, 2^{10} - 1] \rightarrow$ no overflow

n = 11 bits

$$\begin{array}{r} c_{11}=0 \\ c_{10}=1 \\ +990 = 01111011110 + \\ +113 = 00001110001 \\ \hline 10001001111 \end{array}$$

overflow = $c_{11} \oplus c_{10} = 1 \rightarrow$ overflow!
 $990 + 113 = 1103 \notin [-2^{10}, 2^{10} - 1] \rightarrow$ overflow!



To avoid overflow:

n = 12 bits (sign-extension):

$$\begin{array}{r} c_{12}=0 \\ c_{11}=0 \\ +990 = 001111011110 + \\ +113 = 000001110001 \\ \hline +1103 = 010001001111 \end{array}$$

overflow = $c_{12} \oplus c_{11} = 0 \rightarrow$ no overflow
 $+1103 \in [-2^{11}, 2^{11} - 1] \rightarrow$ no overflow

PROBLEM 3 (15 PTS)

- Sign-extension in 2's complement: Whenever we need to increase the number of bits for representing a number, we append the MSB to the left as many times as needed:

$$\begin{aligned} & b_{n-1}b_{n-2} \dots b_0 \equiv b_{n-1} \dots b_{n-1}b_{n-1}b_{n-2} \dots b_0 \\ \text{Examples: } & 00101_2 = 0000101_2 = 2^2 + 2^0 = 5 \\ & 10101_2 = 1110101_2 = -2^4 + 2^2 + 2^0 = -2^6 + 2^5 + 2^4 + 2^2 + 2^0 = -11 \end{aligned}$$

We can think of the sign-extended number as an m -bit number, where $m > n$:

$$b_{n-1} \dots b_{n-1}b_{n-1}b_{n-2} \dots b_0 = k_{m-1} \dots k_n k_{n-1} k_{n-2} \dots k_0$$

- Demonstrate that $b_{n-1}b_{n-2} \dots b_0$ represents the same decimal number as $b_{n-1} \dots b_{n-1}b_{n-1}b_{n-2} \dots b_0$, i.e., demonstrate that sign-extension is correct for any $m > n$.

Useful formula: $\sum_{i=k}^l r^i = \frac{r^{k-r^{l+1}}}{1-r}, r \neq 1$

We need to demonstrate that: $b_{m-1} \dots b_n b_{n-1} b_{n-2} \dots b_0 = b_{n-1} \dots b_{n-1} b_{n-1} b_{n-2} \dots b_0 = b_{n-1} b_{n-2} \dots b_0$, where: $b_i = b_{n-1}, i = n, n + 1, \dots, m - 1$

Using the formula for 2's complement numbers:

$$-2^{m-1}b_{m-1} + \sum_{i=0}^{m-2} 2^i b_i = -2^{n-1}b_{n-1} + \sum_{i=0}^{n-2} 2^i b_i$$

$$-2^{m-1}b_{m-1} + \sum_{i=n-1}^{m-2} 2^i b_i + \sum_{i=0}^{n-2} 2^i b_i = -2^{n-1}b_{n-1} + \sum_{i=0}^{n-2} 2^i b_i \Rightarrow -2^{m-1}b_{m-1} + \sum_{i=n-1}^{m-2} 2^i b_i = -2^{n-1}b_{n-1}$$

$$-2^{m-1}b_{n-1} + b_{n-1} \sum_{i=n-1}^{m-2} 2^i = -2^{n-1}b_{n-1}, \quad \sum_{i=k}^l 2^i = \frac{2^k - 2^{l+1}}{1-2} = 2^{l+1} - 2^k$$



$$-2^{m-1}b_{n-1} + b_{n-1}(2^{m-1} - 2^{n-1}) = -2^{n-1}b_{n-1}$$

$$-2^{m-1}b_{n-1} + 2^{m-1}b_{n-1} - 2^{n-1}b_{n-1} = -2^{n-1}b_{n-1} \therefore -2^{n-1}b_{n-1} = -2^{n-1}b_{n-1}$$


PROBLEM 4 (15 PTS)

- Implement the following functions using i) decoders and ii) multiplexers:
 - $F_a = \bar{X} + \bar{Z} + ZY$
 - $F_b = XY + YZ + XZ$
 - $F_c(X, Y, Z) = \prod(M_1, M_4, M_7)$
 - $F_d = X \oplus Y \oplus Z$


w_2	w_1	w_0		F_a	F_b	F_c	F_d
x	y	z					
0	0	0		1	0	1	0
0	0	1		0	0	0	1
0	1	0		1	0	1	1
0	1	1		1	1	1	0
1	0	0		0	0	0	1
1	0	1		0	1	1	0
1	1	0		0	1	1	0
1	1	1		1	1	0	1

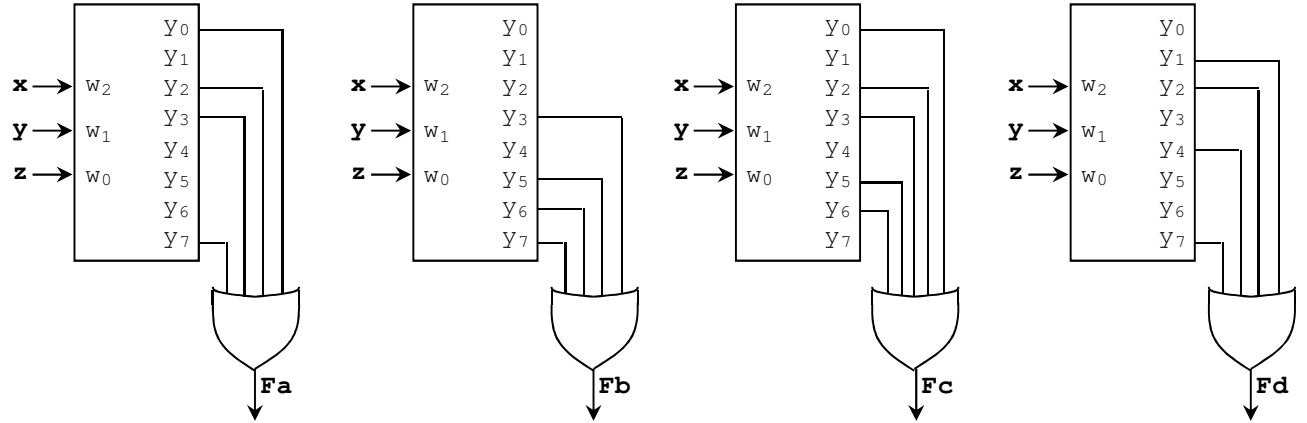 

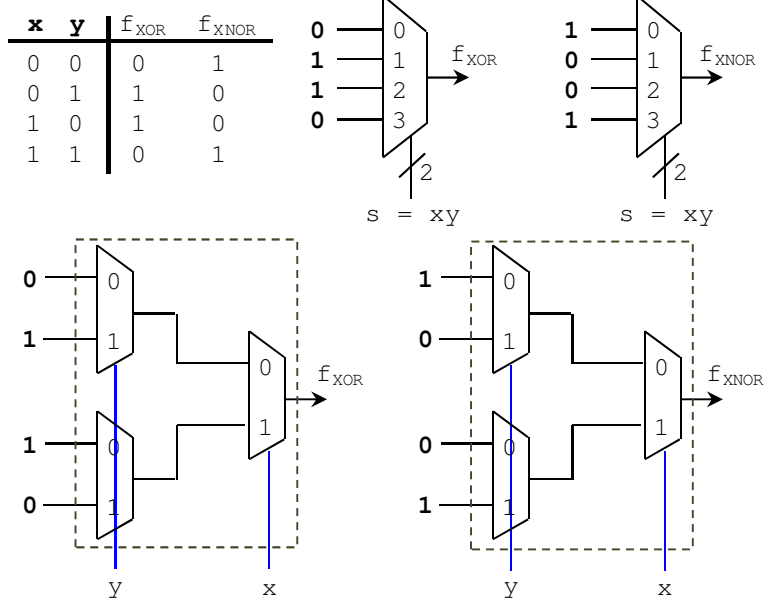- Using only 2-to-1 MUXs, implement the XOR and XNOR gates.





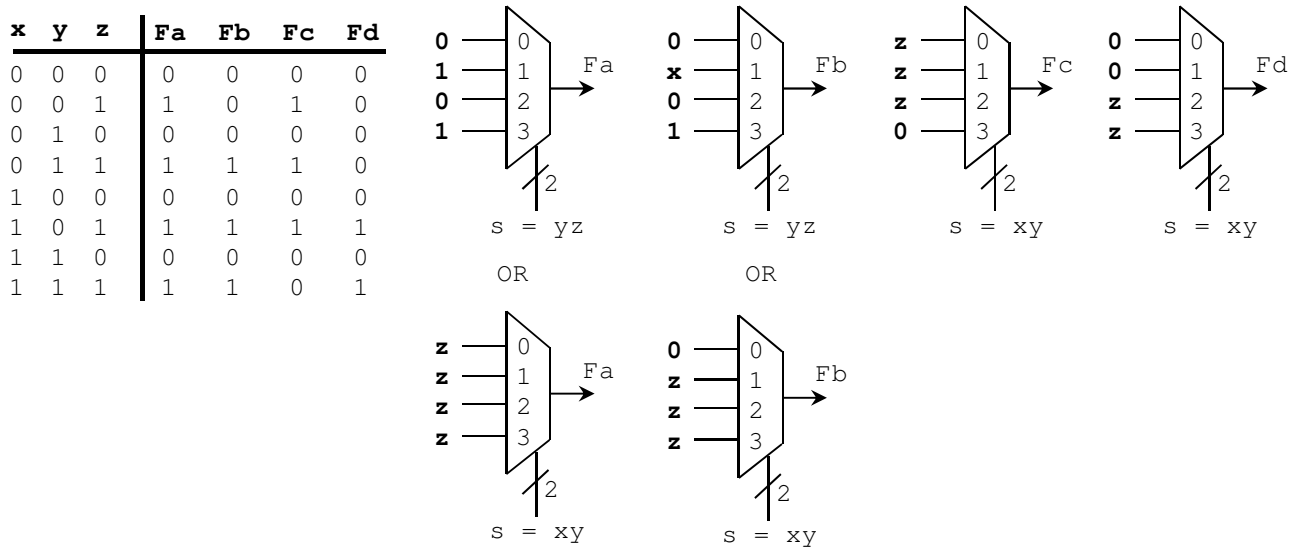- Using only a 4-to-1 MUX, implement the following functions.
 - $F_a(X, Y, Z) = \sum(m_1, m_3, m_5, m_7)$
 - $F_b(X, Y, Z) = \sum(m_3, m_5, m_7)$
 - $F_c(X, Y, Z) = \sum(m_1, m_3, m_5)$
 - $F_d(X, Y, Z) = \sum(m_5, m_7)$



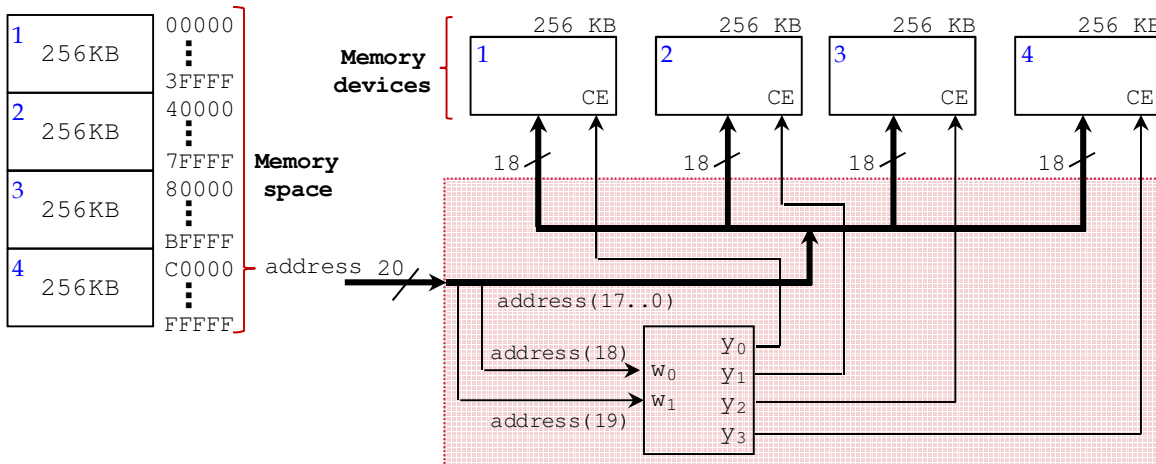 
PROBLEM 5 (10 PTS)

- A 20-bit address line in a μ processor handles up to $2^{20} = 1\text{ MB}$ of addresses, each address containing one-byte of information. We want to connect four 256KB memory chips to the μ processor.
- Sketch the circuit that: i) addresses the memory chips, and ii) enables only one memory chip (via CE: chip enable) when the address falls in the corresponding range. Example: if $address = 0x5FFFF$, \rightarrow only memory chip 2 is enabled ($CE=1$). If $address = 0xD0123$, \rightarrow only memory chip 4 is enabled.




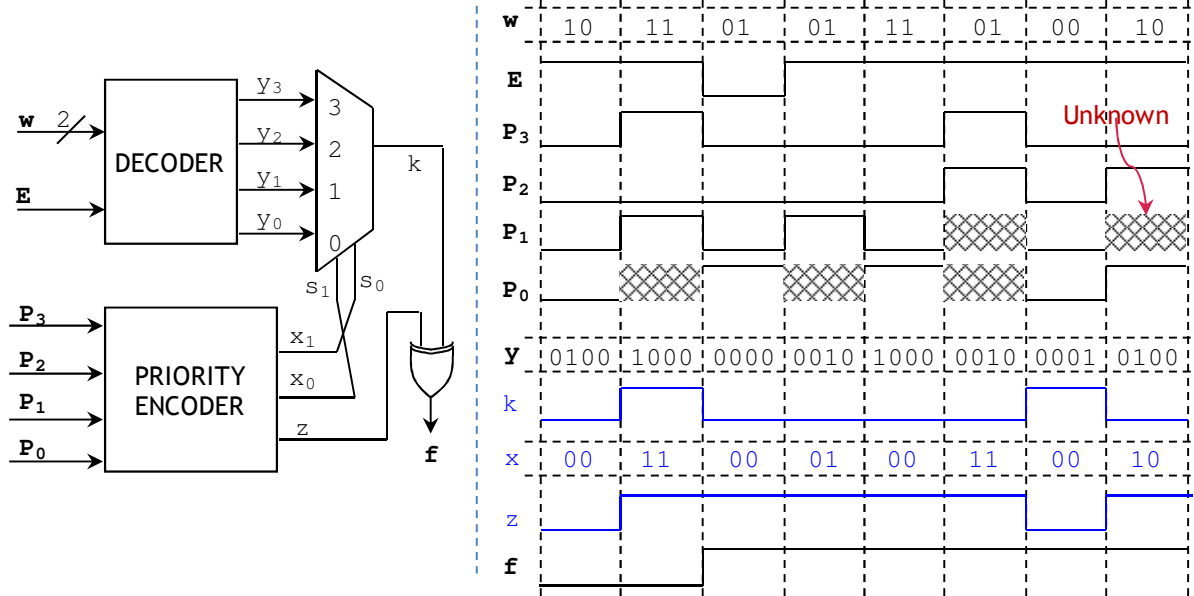PROBLEM 6 (15 PTS)

- Complete the timing diagram of the circuit shown below:



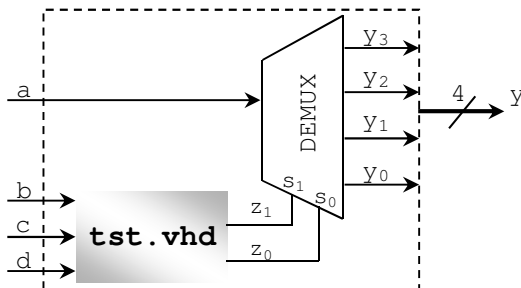
- The following VHDL code corresponds to the shaded circuit. Complete the timing diagram:



```
library ieee;
use ieee.std_logic_1164.all;


entity tst is
  port (b,c,d: in std_logic;
        z: out std_logic_vector(1 downto 0));
end tst;
```
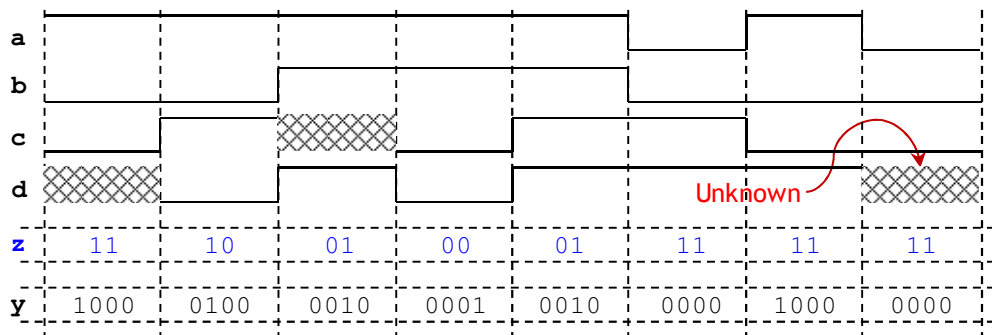
```
architecture bhv of circ is
  signal x, y: std_logic;
begin
  process (b,c,d)
  begin
    z <= c & d;
    if b = '1' then
      case d is
        when '1' => z <= "01";
        when others => z <= "00";
      end case;
    else
      if c = '0' then z <= "11";
      end if;
    end if;
  end process;
end bhv;
```





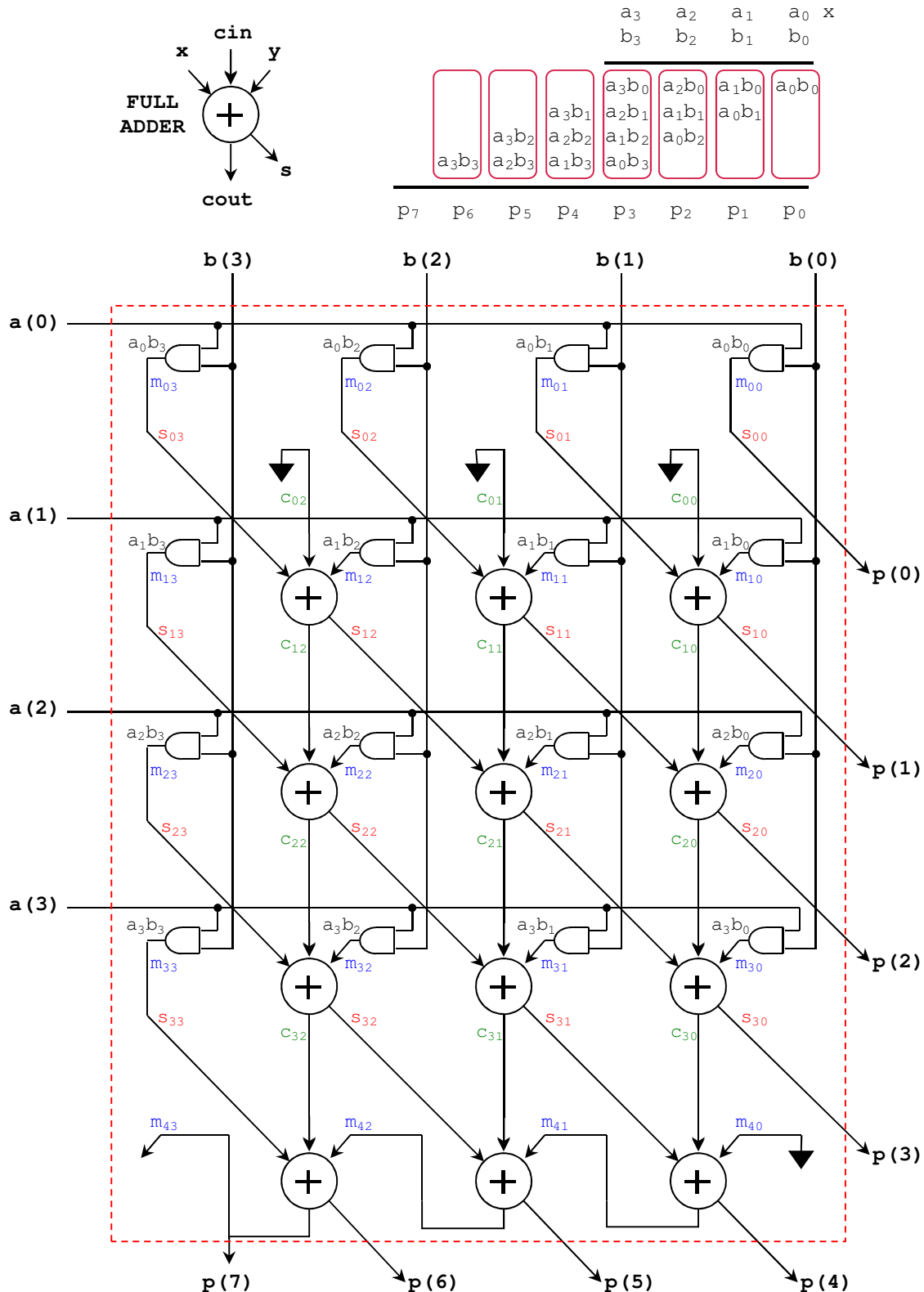
PROBLEM 7 (20 PTS)

- A straightforward implementation of the multiplication operation (for positive or unsigned numbers) is called **Array Multiplier**: the partial products are added up at every column. The figure depicts the hardware implementation for multiplying two unsigned number of 4 bits.



- One of the drawbacks of this approach is the long delay between the input and the output. In the figure, the bits p_7, p_6, p_5, p_4 require the inputs to pass through 4 adders as well as AND gates.

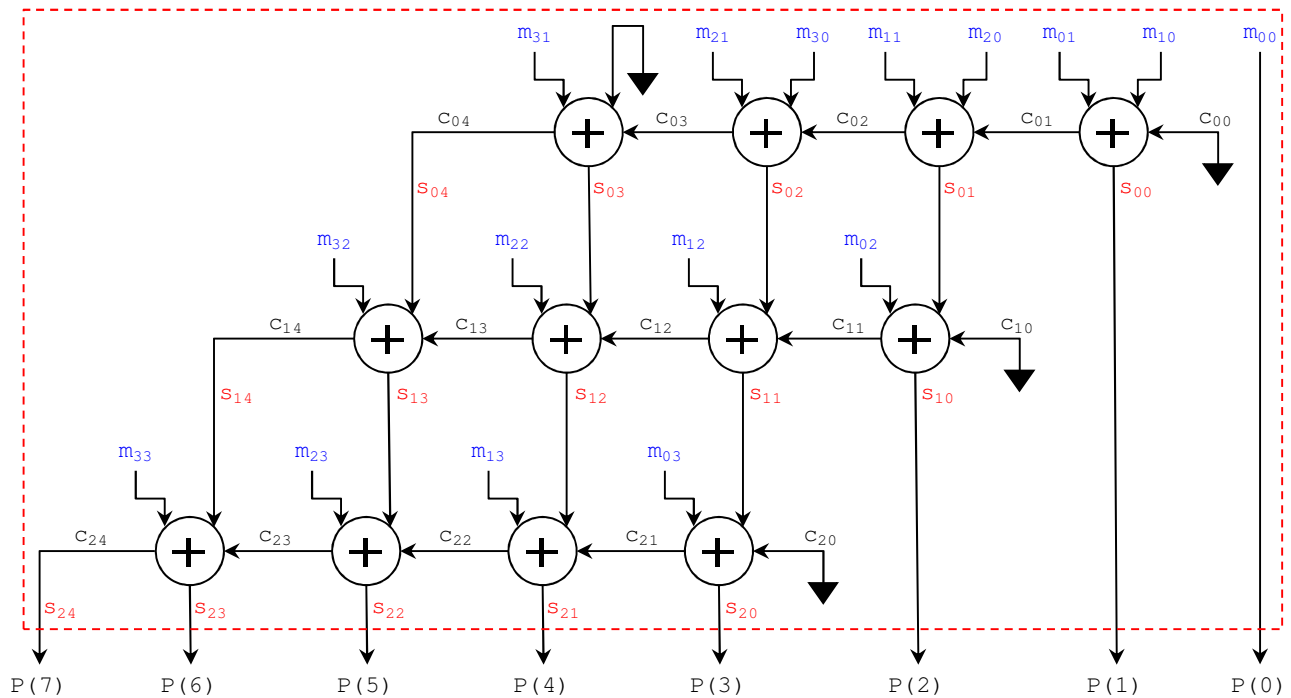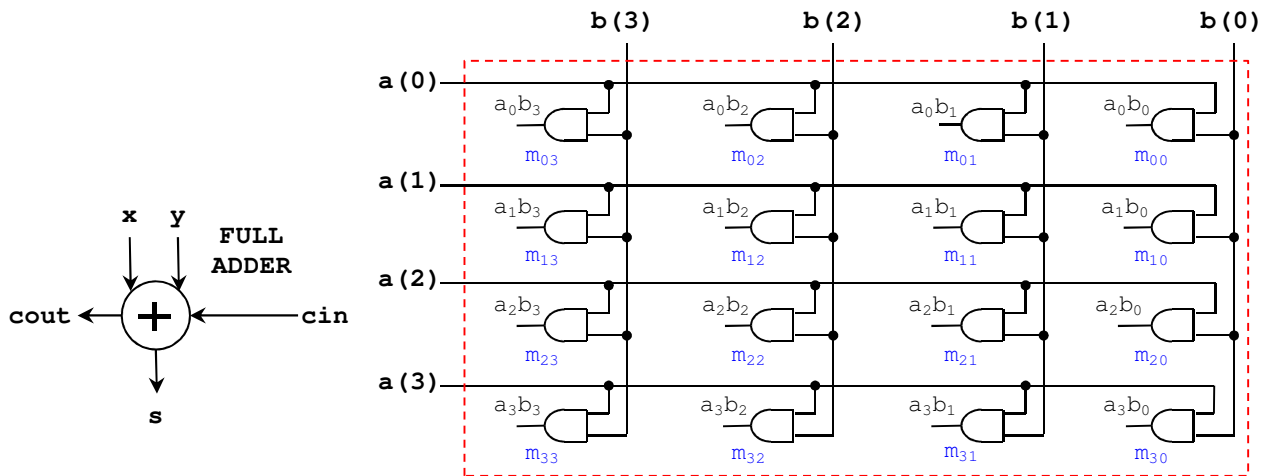 - An alternative implementation, called **Wallace Multiplier**, features a shorter delay between the input and the output. The hardware implementation is more complicated though.
- The figure shows a Wallace multiplier implementation for two unsigned numbers of 4 bits. Note how the addition operation of the 4 rows has been rearranged so that only 2 rows are added up at every stage.



- ✓ Write the VHDL implementation for the multiplication operation of two unsigned numbers of 4 bits using: i) Array Multiplier, and ii) Wallace multiplier. Use the **Structural Description**: create a separate VHDL file for the Full Adder circuit.
- ✓ Simulate both circuits and make sure that they are performing the correct operation.
- ✓ Attach your VHDL code, testbench code, and simulation results.

ARRAY MULTIPLIER:

VHDL Code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity my_mult is
    generic (N: INTEGER:= 4);
    port (A,B: in std_logic_vector (N-1 downto 0);
          P: out std_logic_vector (2*N-1 downto 0));
end my_mult;

architecture structure of my_mult is
    component fulladd
        port( cin, x, y : in std_logic;
              s, cout  : out std_logic);
    end component;

    type my_array is array (natural range <>, natural range <>) of std_logic;
    signal m: my_array(N downto 0, N-1 downto 0);
    signal s: my_array(N-1 downto 0, N-1 downto 0);
    signal c: my_array(N-1 downto 0, N-2 downto 0);

begin

    -- Array of N * (N-1) full adders:
    gi: for i in 0 to N-1 generate -- along rows
        gj: for j in 0 to N-1 generate -- along columns
            m(i,j) <= A(i) and B(j);
            fa: if i /= N-1 and j /= N-1 generate
                fij: fulladd port map (cin => c(i,j), x => s(i,j+1) , y => m(i+1,j),
                                       s => s(i+1,j), cout => c(i+1,j));
            end generate;
            fb: if i = 0 generate
                s(i,j) <= m(i,j);
            end generate;
        end generate;
    end generate;

    m(N,0) <= '0';
    glj: for j in 0 to N-2 generate
        c(0,j) <= '0';
        s(j+1,N-1) <= m(j+1,N-1); -- Column 3 (from rows 1 to N-1)
        P(j+1) <= s(j+1,0);
        flj: fulladd port map (cin => c(N-1,j), x => s(N-1,j+1), y => m(N,j), s => p(N+j),
                               cout => m(N,j+1));
    end generate;

    P(0) <= m(0,0);
    P(2*N-1) <= m(N,N-1);

end structure;
```

Full Adder VHDL Code:

```
library ieee;
use ieee.std_logic_1164.all;

entity fulladd is
    port( cin, x, y : in std_logic;
          s, cout  : out std_logic);
end fulladd;

architecture structure of fulladd is

begin
    s <= x xor y xor cin;
    cout <= (x and y) or (x and cin) or (y and cin);
end structure;
```


Testbench Code:

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
use ieee.std_logic_arith.all;

ENTITY tb_my_mult IS
    generic (N: INTEGER:= 4);
END tb_my_mult;

ARCHITECTURE behavior OF tb_my_mult IS

    -- Component Declaration for the Unit Under Test (UUT)
    COMPONENT my_mult
    PORT(
        A : IN  std_logic_vector(N-1 downto 0);
        B : IN  std_logic_vector(N-1 downto 0);
        P : OUT std_logic_vector(2*N-1 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal A : std_logic_vector(N-1 downto 0) := (others => '0');
    signal B : std_logic_vector(N-1 downto 0) := (others => '0');

    --Outputs
    signal P : std_logic_vector(2*N-1 downto 0);

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: my_mult PORT MAP (
        A => A,
        B => B,
        P => P
    );

    -- Stimulus process
    stim_proc: process
    begin
        -- hold reset state for 100 ns.
        wait for 100 ns;

        -- insert stimulus here
        A <= conv_std_logic_vector(3,N); B <= conv_std_logic_vector (5,N); wait for 20 ns;
        A <= conv_std_logic_vector(12,N); B <= conv_std_logic_vector (11,N); wait for 20 ns;
        A <= conv_std_logic_vector(10,N); B <= conv_std_logic_vector (13,N); wait for 20 ns;
        A <= conv_std_logic_vector(8,N); B <= conv_std_logic_vector (14,N); wait for 20 ns;
        A <= conv_std_logic_vector(10,N); B <= conv_std_logic_vector (8,N); wait for 20 ns;
        A <= conv_std_logic_vector(2*N-1,N); B <= conv_std_logic_vector (2*N-1,N); wait for 20 ns;
        A <= conv_std_logic_vector(0,N); B <= conv_std_logic_vector (0,N); wait for 20 ns;

        wait;
    end process;

END;
```

WALLACE MULTIPLIER (4-BIT):

VHDL Code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity my_wallace_4bit is
    port (A, B: in std_logic_vector (3 downto 0);
          P : out std_logic_vector (7 downto 0));
end my_wallace_4bit;

architecture structure of my_wallace_4bit is

    component fulladd
        port( cin, x, y : in std_logic;
              s, cout  : out std_logic);
    end component;

    type my_array is array (natural range <>, natural range <>) of std_logic;
    signal m: my_array(3 downto 0, 3 downto 0);
    signal c: my_array(2 downto 0, 4 downto 0);
    signal s: my_array(2 downto 0, 4 downto 0);

begin

    gi: for i in 0 to 3 generate -- along rows
        gj: for j in 0 to 3 generate -- along columns
            m(i,j) <= A(i) and B(j);
        end generate;
    end generate;

    c(0,0) <= '0'; c(1,0) <= '0'; c(2,0) <= '0';
    s(0,4) <= c(0,4); s(1,4) <= c(1,4); s(2,4) <= c(2,4);

    -- First Layer
    f00: fulladd port map (cin => c(0,0), x => m(0,1), y => m(1,0), s => s(0,0), cout => c(0,1));
    f01: fulladd port map (cin => c(0,1), x => m(1,1), y => m(2,0), s => s(0,1), cout => c(0,2));
    f02: fulladd port map (cin => c(0,2), x => m(2,1), y => m(3,0), s => s(0,2), cout => c(0,3));
    f03: fulladd port map (cin => c(0,3), x => m(3,1), y => '0', s => s(0,3), cout => c(0,4));

    -- Second Layer
    f10: fulladd port map (cin => c(1,0), x => m(0,2), y => s(0,1), s => s(1,0), cout => c(1,1));
    f11: fulladd port map (cin => c(1,1), x => m(1,2), y => s(0,2), s => s(1,1), cout => c(1,2));
    f12: fulladd port map (cin => c(1,2), x => m(2,2), y => s(0,3), s => s(1,2), cout => c(1,3));
    f13: fulladd port map (cin => c(1,3), x => m(3,2), y => s(0,4), s => s(1,3), cout => c(1,4));

    -- Third Layer
    f20: fulladd port map (cin => c(2,0), x => m(0,3), y => s(1,1), s => s(2,0), cout => c(2,1));
    f21: fulladd port map (cin => c(2,1), x => m(1,3), y => s(1,2), s => s(2,1), cout => c(2,2));
    f22: fulladd port map (cin => c(2,2), x => m(2,3), y => s(1,3), s => s(2,2), cout => c(2,3));
    f23: fulladd port map (cin => c(2,3), x => m(3,3), y => s(1,4), s => s(2,3), cout => c(2,4));

    P(0) <= m(0,0);
    P(1) <= s(0,0);
    P(2) <= s(1,0);
    P(3) <= s(2,0);
    P(4) <= s(2,1);
    P(5) <= s(2,2);
    P(6) <= s(2,3);
    P(7) <= s(2,4);

end structure;
```

Testbench Code:

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
use ieee.std_logic_arith.all;

ENTITY tb_my_wallace_4bit IS
END tb_my_wallace_4bit;

ARCHITECTURE behavior OF tb_my_wallace_4bit IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT my_wallace_4bit
    PORT(
        A : IN  std_logic_vector(3 downto 0);
        B : IN  std_logic_vector(3 downto 0);
        P : OUT std_logic_vector(7 downto 0)
    );
    END COMPONENT;

    --Inputs
    signal A : std_logic_vector(3 downto 0) := (others => '0');
    signal B : std_logic_vector(3 downto 0) := (others => '0');

    --Outputs
    signal P : std_logic_vector(7 downto 0);

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: my_wallace_4bit PORT MAP (
        A => A,
        B => B,
        P => P
    );

    -- Stimulus process
    stim_proc: process
    begin
        -- hold reset state for 100 ns.
        wait for 100 ns;
        -- insert stimulus here
        lj: for i in 0 to 15 loop
            A <= conv_std_logic_vector(i,4);
            lj: for j in 0 to 15 loop
                B <= conv_std_logic_vector(j,4); wait for 20 ns;
            end loop;
        end loop;
        A <= x"0"; B <= x"0"; wait for 20 ns;

        wait;
    end process;

END;
```