

# DIGITAL LOGIC DESIGN


## VHDL Coding for FPGAs

### Unit 4



#### ✓ *STRUCTURAL DESCRIPTION*

- Hierarchical design: port-map, for-generate, if-generate.
- Examples: Adder, multiplier, ALU, Look-up Table.
- Introduction to Parametric Coding.

# ✓ STRUCTURAL DESCRIPTION

 

  - It is the generalization of the Concurrent Description. The circuits are described via interconnection of its subcircuits. This subcircuits can be described in concurrent code and/or sequential code.
- **Example:** Multiplexor 2-to-1.




- This case is trivial, since the interconnection is realised via logic operators, but nevertheless it is an example of structural description.


# ✓ STRUCTURAL DESCRIPTION

 - **Example:** 4-to-16 decoder

- We can describe this decoder in an structured way based on 2-to-4 decoders.
  - However, we can also describe the 4-to-16 decoder using the with-select statement.




# ✓ STRUCTURAL DESCRIPTION

 


RECRLab

Reconfigurable Computing Research Laboratory

 - **Example:** DLX Processor
- In this type of systems, it is best to describe each component first, then assemble them to make the large system.
- We do not need to see such large system to realise the importance of the Structural Description.



# ✓ STRUCTURAL DESCRIPTION

 

- Many systems can be described entirely in one single block: we can use the behavioral description, and/or concurrent statements (with-select, when-else).
- However, it is advisable not to abuse of this technique since it makes: i) the code less readable, ii) the circuit verification process more cumbersome, and iii) circuits improvements less evident.
- The structural description allows for a hierarchical design: we can 'see' the entire circuit as the pieces it is made of, then identify critical points and/or propose improvements on each piece.
- It is always convenient to have basic building blocks from which we can build more complex circuits. This also allows building block (or sub-system) to be re-used in a different circuit.


# ✓ STRUCTURAL DESCRIPTION



RECRLab


Reconfigurable Computing Research Laboratory

 - Example: 4-bit add/sub for numbers in 2's complement
- The circuit can be described in one single block. However, it is best to describe the Full Adder as a block in a separate file (`full_add.vhd`), then use as many full adders to build the 4-bit adder.
- The place where we use and connect as many full adders as desired, and possibly add extra circuitry is called the ‘top file’ (`my_addsub.vhd`). This creates a hierarchy of files in the VHDL project:




`my_addsub.vhd`

`full_add.vhd`

 

# ✓ 4-bit 2's complement Adder

 

- Full Adder: VHDL Description (fulladd.vhd):


```
library ieee;
use ieee.std_logic_1164.all;

entity fulladd is
  port ( cin, x, y: in std_logic;
         s, cout: out std_logic);
end fulladd;


architecture struct of fulladd is
begin

  s <= x xor y xor cin;
  cout <= (x and y) or (x and cin) or (y and cin);

end struct;
```

 

# ✓ 4-bit 2's complement Adder

 

- Top file (my\_addsub.vhd): We need 4 full adders block and extra logic circuitry.

```
library ieee;
use ieee.std_logic_1164.all;

entity my_addsub is
    port ( addsub: in std_logic;
           x,y: in std_logic_vector(3 downto 0);
           s: out std_logic_vector(3 downto 0);
           cout, overflow: out std_logic);
end my_addsub;

architecture struct of my_addsub is
    component fulladd
        port ( cin, x, y: in std_logic;
               s, cout: out std_logic);
    end component;

    signal c: std_logic_vector(4 downto 0);
    signal yt: std_logic_vector(3 downto 0);

begin -- continued on next page
```

We copy what  
is in the entity of  
full\_add.vhd

# ✓ 4-bit 2's complement Adder

- Here, we:
  - Insert the required extra circuitry (xor gates and I/O connections).
  - Instantiate the full adders and interconnect them (using the **port map** statement)

```
-- continuation from previous page
```


```
c(0) <= addsub; cout <= c(4);  
overflow <= c(4) xor c(3);
```

```
yt(0) <= y(0) xor addsub; yt(1) <= y(1) xor addsub;  
yt(2) <= y(2) xor addsub; yt(3) <= y(3) xor addsub;
```

```
f0: fulladd port map(cin=>c(0),x=>x(0),y=>yt(0),s=>s(0),cout=>c(1));  
f1: fulladd port map(cin=>c(1),x=>x(1),y=>yt(1),s=>s(1),cout=>c(2));  
f2: fulladd port map(cin=>c(2),x=>x(2),y=>yt(2),s=>s(2),cout=>c(3));  
f3: fulladd port map(cin=>c(3),x=>x(3),y=>yt(3),s=>s(3),cout=>c(4));
```

```
end struct;
```

# ✓ 4-bit 2's complement Adder

 


Reconfigurable Computing Research Laboratory

- Use of ‘*port map*’ statement:

```
port map (signal in full adder => signal in top file, ...)
```

- Instantiating and connecting the first full adder:
 
```
f0: fulladd port map (cin=>c(0), x=>x(0), y=>y_t(0), s=>s(0), cout=>c(1));
```




# ✓ 4-bit 2's complement Adder

- Use of ‘*port map*’ statement:


`port map (signal in full adder => signal in top file, ...)`

- Instantiating and connecting the second full adder:
 
`f1: fulladd port map (cin=>c(1), x=>x(1), y=>y_t(1), s=>s(1), cout=>c(2));`



# ✓ 4-bit 2's complement Adder

 


Reconfigurable Computing Research Laboratory

- Use of ‘*port map*’ statement:


`port map (signal in full adder => signal in top file, ...)`

- Instantiating and connecting the third full adder:
 
```
f2: fulladd port map (cin=>c(2),x=>x(2),y=>yt(2),s=>s(2),cout=>c(3));
```



# ✓ 4-bit 2's complement Adder

 


Reconfigurable Computing Research Laboratory


- Use of ‘*port map*’ statement:

```
port map (signal in full adder => signal in top file, ...)
```

- Instantiating and connecting the fourth full adder:
 
```
f3: fulladd port map (cin=>c(3),x=>x(3),y=>y t(3),s=>s(3),cout=>c(4));
```



 

# ✓ FOR-GENERATE Statement

- In the 4-bit adder example, if we wanted to use say 8 bits, we would need to instantiate 8 full adders and write 8 port map statements.
- Instantiating components can be a repetitive task, thus the **for-generate** statement is of great help here:

```
yt(0) <= y(0) xor addsub; yt(1) <= y(1) xor addsub;  
yt(2) <= y(2) xor addsub; yt(3) <= y(3) xor addsub;  
  
f0: fulladd port map(cin=>c(0),x=>x(0),y=>yt(0),s=>s(0),cout=>c(1));  
f1: fulladd port map(cin=>c(1),x=>x(1),y=>yt(1),s=>s(1),cout=>c(2));  
f2: fulladd port map(cin=>c(2),x=>x(2),y=>yt(2),s=>s(2),cout=>c(3));  
f3: fulladd port map(cin=>c(3),x=>x(3),y=>yt(3),s=>s(3),cout=>c(4));  
  
-- continuation from previous page  
c(0) <= addsub; cout <= c(4);  
overflow <= c(4) xor c(3);  
  
gi: for i in 0 to 3 generate  
    yt(i) <= y(i) xor addsub;  
    fi: fulladd port map(cin=>c(i),x=>x(i),y=>yt(i),s=>s(i),cout=>c(i+1));  
end generate;  
end struct;
```



# ✓ INTRODUCTION TO PARAMETRIC CODING



Reconfigurable Computing Research Laboratory

- N-bit adder/subtractor. We can choose the value of N in the entity.
- The architecture code is tweaked so as to make it parametric.

**Example:** Parametric N-bit adder/subtractor in 2's complement:

➤ **my\_addsub.zip:**  
my\_addsub.vhd,  
fulladd.vhd  
tb\_my\_addsub.vhd,  
my\_addsub.xdc

```
library ieee;
use ieee.std_logic_1164.all;

entity my_addsub is
    generic (N: INTEGER:= 4);
    port( addsub      : in std_logic;
          x, y       : in std_logic_vector (N-1 downto 0);
          s         : out std_logic_vector (N-1 downto 0);
          overflow   : out std_logic;
          cout       : out std_logic);
end my_addsub;

architecture structure of my_addsub is
component fulladd
    port( cin, x, y : in std_logic;
          s, cout   : out std_logic);
end component;

signal c: std_logic_vector (N downto 0);
signal yx: std_logic_vector (N-1 downto 0);
begin
    c(0) <= addsub; cout <= c(N);
    overflow <= c(N) xor c(N-1);
    gi: for i in 0 to N-1 generate
        yx(i) <= y(i) xor addsub;
    fi: fulladd port map (cin=>c(i),x=>x(i),y=>yx(i),
                           s=>s(i),cout=>c(i+1));
    end generate;
end structure;
```

# ✓ INTRODUCTION TO PARAMETRIC CODING



Reconfigurable Computing Research Laboratory

- **Example:** N-bit adder/subtractor.

- **Testbench:** Use of '**for loop**' inside the stimulus process to generate all possible input combinations.

- **Parametric Testbench:** It depends on **N**, which must match the hardware description

```
y<="0000"; x<="0000"; wait for 10 ns;
y<="0000"; x<="0001"; wait for 10 ns;
...
y<="0000"; x<="1111"; wait for 10 ns;
y<="0001"; x<="0000"; wait for 10 ns;
y<="0001"; x<="0001"; wait for 10 ns;
...
y<="0001"; x<="1111"; wait for 10 ns;
...
```


```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all; -- for conv_std_logic_vector

entity tb_my_addsub is
    generic (N: INTEGER:= 4); -- must match the HW description
end tb_my_addsub;

architecture structure of my_addsub is
    component my_addsub -- Do not do 'generic map' in testbench
        port( addsub      : in std_logic;
              x, y       : in std_logic_vector (N-1 downto 0);
              s          : out std_logic_vector (N-1 downto 0);
              overflow,cout : out std_logic);
    end component;
    -- Inputs
    signal addsub: std_logic:='0';
    signal x,y: std_logic_vector (N-1 downto 0):= others => '0';
    -- Outputs
    signal overflow, cout: std_logic;
    signal s: std_logic_vector (N-1 downto 0);

begin
    uut: my_addsub port map (addsub, x, y, s, overflow, cout);
    st: process
    begin
        wait for 100 ns;
        addsub <= '0'; -- Pick '1' to test subtraction
        gi: for i in 0 to 2**N-1 loop
            y <= conv_std_logic_vector(i,N);
            gj: for j in 0 to 2**N-1 loop
                x <= conv_std_logic_vector(j,N); wait for 10 ns;
                end loop;
            end loop;
        wait;
    end process;
end;
```

# ✓ Example: 4-bit array multiplier

 

RECRLab

Reconfigurable Computing Research Laboratory

- Interesting example of structural description. By connecting full adders and AND gates, we build this array multiplier.


- We parameterize the circuit with 'if-generate', 'for-generate', and the use of arrays in VHDL.

- Testbench: we use `conv_std_logic_vector` to specify input values


Parametric N-bit array multiplier:

➤ `my_mult.zip`:
 
`my_mult.vhd.vhd`,  
`fulladd.vhd`,  
`tb_my_mult.vhd`,  
`my_mult.xdc`




# ✓ Example: Arithmetic Logic Unit

 

- This circuit executes two types of operations: logic (or bit-wise) and arithmetic.
- The arithmetic unit and the logic unit are described in different VHDL files.
- The arithmetic unit relies heavily on the parametric adder/subtractor unit.
- The VHDL code is parameterized so as to allow for two N-bit operands.
- The 'sel' inputs selects the operation to be carried on (as per the table).

➤ [my\\_alu.zip](#):



 
[my\\_alu.vhd](#),  
[my\\_alu\\_arith.vhd](#),  
[my\\_alu\\_logic.vhd](#),  
[my\\_addsub.vhd](#),  
[fulladd.vhd](#)  
[tb\\_my\\_alu.vhd](#)



sel	Operation	Function	Unit
0 0 0 0	$y \leq a$	Transfer 'a'	Arithmetic
0 0 0 1	$y \leq a + 1$	Increment 'a'	
0 0 1 0	$y \leq a - 1$	Decrement 'a'	
0 0 1 1	$y \leq b$	Transfer 'b'	
0 1 0 0	$y \leq b + 1$	Increment 'b'	
0 1 0 1	$y \leq b - 1$	Decrement 'b'	
0 1 1 0	$y \leq a + b$	Add 'a' and 'b'	
0 1 1 1	$y \leq a - b$	Subtract 'b' from 'a'	
1 0 0 0	$y \leq \text{NOT } a$	Complement 'a'	
1 0 0 1	$y \leq \text{NOT } b$	Complement 'b'	
1 0 1 0	$y \leq a \text{ AND } b$	AND	Logic
1 0 1 1	$y \leq a \text{ OR } b$	OR	
1 1 0 0	$y \leq a \text{ NAND } b$	NAND	
1 1 0 1	$y \leq a \text{ NOR } b$	NOR	
1 1 1 0	$y \leq a \text{ XOR } b$	XOR	
1 1 1 1	$y \leq a \text{ XNOR } b$	XNOR	
   
# ✓ Example: 6-to-6 LUT

- The LUT contents (64 bytes) are specified as a set of 6 parameters. These 6 parameters are 'generics' in the VHDL code.
- Note that if the parameters are modified, we will get a different circuit that needs to be re-synthesized. In other words, the LUT contents are NOT inputs to the circuit.



➤ **my6to6LUT.zip:** my6to6LUT.vhd, my6to1LUT.vhd, my5to1LUT.vhd, my4to1LUT.vhd, tb\_my6to6LUT.vhd, my6to6LUT.ucf