

# DIGITAL LOGIC DESIGN


## VHDL Coding for FPGAs

### Unit 8

#### ✓ **PARAMETRIC CODING**

- Techniques: generic input size, for-generate, if-generate, conv\_integer.
- Custom-defined arrays, functions, and packages.
- Examples: vector mux, vector demux, vectordemux (2D input array), barrel shifter, 2D convolution kernel.

# ✓ Techniques: Generic input size

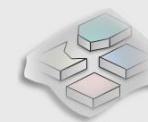


## ▪ Example: Tri-state buffer

Input data: N bits

Output data: N bits

Number of 3-state buffers required: N

 

```
library ieee;
use ieee.std_logic_1164.all;

entity buffer_tri is
  generic (N: INTEGER:= 4);
  port ( OE: in std_logic;
         A: in std_logic_vector(N-1 downto 0);
         F: out std_logic_vector(N-1 downto 0));
end buffer_tri;

architecture bhv of buffer_tri is
begin
  with OE select
    F <= A when '1',
    (others => 'Z') when others;
end bhv;
```

➤ **buffer\_tri.zip:**  
buffer\_tri.vhd,  
tb\_buffer\_tri.vhd


# ✓ Techniques: for-generate

## ▪ Example: Binary to Gray Code converter

Input data: N bits

Output data: N bits

Number of XOR gates required: N-1

 

```
library ieee;
use ieee.std_logic_1164.all;

entity bin2gray is
  generic (N: INTEGER:= 8);
  port ( B: in std_logic_vector(N-1 downto 0);
         G: out std_logic_vector(N-1 downto 0));
end bin2gray;

architecture bhv of bin2gray is
begin
  G(N-1) <= B(N-1);
  pg: for i in N-2 downto 0 generate
    G(i) <= B(i) xor B(i+1);
  end generate;
end bhv;
```


## Generic Testbench:

Parameter N used to generate all possible combinations

### ➤ bin2gray.zip:

bin2gray.vhd,  
tb\_bin2gray.vhd

# ✓ Techniques: conv\_integer

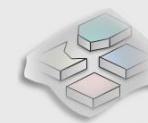

RECRLab

Reconfigurable Computing Research Laboratory

## ▪ Example: MUX N-to-1

Input data: N bits.      Output data: 1 bit

Number of selector bits: calculated using real functions.

The MUX output is selected via indexing.

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;
use ieee.math_real.log2;
use ieee.math_real.ceil;

entity muxNto1 is
    generic (N: INTEGER:= 8);
    port (D: in std_logic_vector (N-1 downto 0);
          sel:in std_logic_vector(integer(ceil(log2(real(N))))-1 downto 0);
          y: out std_logic);
end muxNto1;

architecture structure of muxNto1 is
begin
    y <= D(conv_integer(sel));
end structure;
```


➤ muxNto1.zip:

muxNto1.vhd,

tb\_muxNto1.vhd

OAKLAND  
UNIVERSITY™

# ✓ Techniques: if-generate

 

- This is useful if we want to pick between different pieces of hardware. Only one hardware piece will be implemented.
- **Example: Johnson/Ring Counter.** At Synthesis, we select which counter is to be implemented. It can't be changed at running time.


```
library ieee;
use ieee.std_logic_1164.all;

entity my_johnson_ring_counter is
    generic (COUNTER: STRING:="JOHNSON"; -- "RING"
             N: INTEGER:= 4);
    port (clock, resetn, E: in std_logic;
          Q: out std_logic_vector (N-1 downto 0));
end my_johnson_ring_counter;

architecture Behavioral of my_johnson_ring_counter is
    component my_johnson_counter is
        generic (N: INTEGER:= 4);
        port (clock, resetn, E: in std_logic;
              Q: out std_logic_vector (N-1 downto 0));
    end component;
    component my_ring_counter is
        generic (N: INTEGER:= 4);
        port (clock, startn, E: in std_logic;
              Q: out std_logic_vector (N-1 downto 0));
    end component;
    ...

```

 - Here, the parameter COUNTER="JOHNSON" → only the block **my\_johnson\_counter** will be implemented.



```
    ...
begin
    jo: if COUNTER = "JOHNSON" generate
        jc: my_johnson_counter generic map (N => N)
            port map (clock=>clock,resetn=>resetn,E=>E,Q=>Q);
    end generate;
    ri: if COUNTER = "RING" generate
        rc: my_ring_counter generic map (N => N)
            port map (clock=>clock,startn=>resetn,E=>E,Q=>Q);
    end generate;
end Behavioral;
```

- **my\_johnson\_ring\_counter.zip:**  
my\_johnson\_counter.vhd,  
my\_ring\_counter.vhd, dffe.vhd  
tb\_my\_johnson\_ring\_counter.vhd

# ✓ Techniques: if-generate

- **Example: Unsigned/signed Multiplier.** At Synthesis, we can select the representation of the operands: signed (2C), or unsigned. The representation cannot be altered at running time.


```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use ieee.std_logic_arith.all;

entity my_mult is
    generic (NA: INTEGER:= 4;
              NB: INTEGER:= 4;
              REP: STRING:="SIGNED");
    port (A: in std_logic_vector (NA-1 downto 0);
          B: in std_logic_vector (NB-1 downto 0);
          P: out std_logic_vector (NA+NB-1 downto 0));
end my_mult;

architecture structure of my_mult is
begin
    fa: if REP = "UNSIGNED" generate
        P <= unsigned(A)*unsigned(B);
    end generate;
    fb: if REP = "SIGNED" generate
        P <= signed(A)*signed(B);
    end generate;
end structure;
```


- **simple\_mult.zip:**  
my\_mut.vhd, tb\_my\_mult.vhd

# ✓ Custom-defined arrays

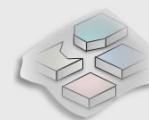


- VHDL allows for custom-defined data types, like **custom arrays**:
- They are defined in the architecture. Here, N, B, M are constants.
- Linear Array of vectors: It can also be seen as a 2D array of bits.
 
```
type chunk is array (N-1 downto 0) of std_logic_vector (B-1 downto 0);  
signal data: chunk;
```



- Matrix of Vectors: It can also be seen as a 3D array of bits.

 
```
type chunk2D is array (N-1 downto 0, M-1 downto 0) of std_logic_vector (B-1  
downto 0);  
signal vf: chunk2D;
```




- Unconstrained array type: The signal definition will constrain the array

```
type chunk is array (natural range <>) of std_logic_vector (B-1 downto 0);  
signal data: chunk(N-1 downto 0);
```

# ✓ Custom-defined arrays

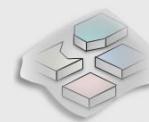

 - **Example: Vector mux:** Input:  $N \times B$  bits. For simplicity, we convert the input into an  $N$ -element array of  $B$  bits per element:  $D_i$



# ✓ Custom-defined arrays



# RECRLab

Reconfigurable Computing Research Laboratory

- Example: Vector MUX → Generic testbench.
- Arrays can be displayed in the Simulation Window.

```
...
ENTITY tb_vectormux IS
  generic (B: INTEGER:= 8;
           N: INTEGER:= 16);
  end tb_vectormux;

ARCHITECTURE behavior OF tb_vectormux IS
  component vectormux
    port ( D: in std_logic_vector (B*N -1 downto 0);
           sel: in std_logic_vector (integer (ceil(log2(real(N)))) -1 downto 0);
           F: out std_logic_vector (B-1 downto 0));
  end component;

  signal D: std_logic_vector(B*N-1 downto 0);
  signal sel: std_logic_vector ( NSEL -1 downto 0):= (others => '0');
  signal F: std_logic_vector (B-1 downto 0);

For easy data feeding, we define arrays inside the testbench
  type chunk is array (N-1 downto 0) of std_logic_vector(B-1 downto 0);
  signal Dv: chunk;
begin
  -- Converting std_logic_vector to chunk:
  st: for i in 0 to N-1 generate
    D(B*(N-i) - 1 downto B*(N - (i+1)) ) <= Dv(i);
  end generate;

  uut: vectormux port map (D, sel, F);
  tb : PROCESS
  BEGIN
    bi: for i in 0 to N - 1 loop
      bj: for j in 0 to N-1 loop
        sel <= conv_std_logic_vector (j, NSEL);
        Instead of input D, we provide data as Dv(i): Dv(j) <= conv_std_logic_vector (i*N +j,B); wait for 20 ns;
        end loop;
      end loop;
      wait;
    END PROCESS tb;
  END;
```

They must match those of vectormux.vhd

Each element Dv(i) of array Dv is assigned to vector D

➤ **vectormux.zip:**  
vectormux.vhd,  
tb\_vectormux.vhd

# ✓ Custom arrays and functions

- **Example: Vector demux:** We use a custom function `myconv_integer(data)`.
- **Function:** Subprogram that computes a result to be used in expressions.  
...

```
entity vectordemux is
    generic (B: INTEGER:= 8; -- bitwidth of each output
             N: INTEGER:= 16); -- number of outputs
    port (F: out std_logic_vector (B*N -1 downto 0);
          sel: in std_logic_vector (integer(ceil(log2(real(N))))-1 downto 0);
          D: in std_logic_vector (B-1 downto 0));
end vectordemux;

architecture structure of vectormux is
    function myconv_integer(data: in std_logic_vector) return integer is
        variable result: integer := 0;
    begin
        for i in data'range loop -- Loop thru all bits
            if data(i) = '1' then
                result:= result + 2**i;
            end if;
        end loop;
        return result;
    end function myconv_integer;
    type chunk is array (N-1 downto 0) of std_logic_vector (B - 1 downto 0);
    signal Fi: chunk;
```


unconstrained array:

→ No need to know the exact width

It does the same job  
as `conv_integer(unsigned(data))`

It does simple data conversion, it  
DOES NOT represent a circuit


# ✓ Custom arrays and functions

 

RECRLab

Reconfigurable Computing Research Laboratory

 - **Example: Vector demux:** Input has B bits. For simplicity, we define the output data as an N-element array of B bits per element:  $F_i$ .
- **Array slicing:** We can assign  $F_i(1)(2), F_i(1)(3 \text{ downto } 0)$ .



```
begin
  process (sel,D)
  begin
    bi: for i in 0 to N-1 loop
      Fi(i) <= (others => '0');
    end loop;
    Fi(myconv_integer(sel)) <= D;
  end process;
```

```
-- Converting chunk to std_logic_vector:
```

```
st: for i in 0 to N-1 generate
  F(B*(N-i)-1 downto B*(N-(i+1))) <= Fi(i);
end generate;
end structure;
```

➤ **vectordemux.zip:**  
vectordemux.vhd,  
tb\_vectordemux.vhd

# ✓ Custom arrays and packages



- **Packages:** We can define custom data types, functions, and components.

- We can define arrays of vectors and use them in any design file. However, the size of the array and of the elements is fixed:

```
type myar is array (7 downto 0) of std_logic_vector (3 downto 0);
```

- Generic data types are not allowed in VHDL-1993:

```
type myar is array (N-1 downto 0) of std_logic_vector (B-1 downto 0);
```

We cannot define this in a package file as N and B are unknown.

- We can define unconstrained arrays (1D, 2D) of a bit or a fixed bitwidth:

```
type u1D is array (natural range <>) of std_logic_vector (3 downto 0);
```

```
type u2D is array (natural range <>, natural range <>) of std_logic_vector (7 downto 0);
```

When we use these datatypes in a design file, we define the array size:

```
generic (N: integer:= 16);
```


port ( data\_in: u1D (N-1 downto 0)); → This is an array of N 4-bit vectors

This is useful, but the data type u1D still has fixed-size (4-bit) elements.

- Special custom array (std\_logic\_2d) 2D array of one bit. This allows us to use this data type in any design file and to pass 2D generic data:

```
type std_logic_2d is array (natural range <>, natural range <>) of std_logic;
```

# ✓ Custom arrays and packages

 

- **Example: Vector Mux 2D with std\_logic\_2d:**
- Package file: `pack_xtras.vhd`, here we define: the datatype `std_logic_2d`, the function `ceil_log2()`, and two hardware components.
  - With `std_logic_2d`, we can have a generic vector mux with a 2D input.

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.std_logic_arith.all;

package pack_xtras is

    type std_logic_2d is array (natural RANGE <>, NATURAL RANGE <>) of std_logic; ────────── Custom datatype definition

    function ceil_log2(data: in integer) return integer; ────────── Custom function declaration

    component dffe
        port ( d, clk, ena : in STD_LOGIC;
               clrn,prn: in std_logic:= '1';
               q : out STD_LOGIC);
    end component;

    component my_rege
        generic (N: INTEGER:= 4);
        port (clock, resetn, E, sclr: in std_logic;
              D: in std_logic_vector (N-1 downto 0);
              Q: out std_logic_vector (N-1 downto 0));
    end component;

end package pack_xtras;

package body pack_xtras is


    function ceil_log2(data: in integer) return integer is
        variable i, valor: integer;
    begin
        i:= 0; valor:= data;
        while valor /= 1 loop
            valor := valor - (valor/2);
            i:= i + 1;
        end loop;
        return i;
    end function ceil_log2;
end package body pack_xtras;
```

Components 'dff' and 'my\_rege' declaration:  
These files must exist in the project if we plan to use these components.

When using the package 'pack\_xtras', there is no need to declare these components in the architecture portion.

Function description.  
This function computes the result at synthesis time.

# ✓ Custom arrays and packages

 


- **Example: Vector Mux 2D with std\_logic\_2d:**
- **Array Slicing** with std\_logic\_2d: not possible, we can only assign one bit at a time: D(1,B-1).

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;

library work;
use work.pack_xtras.all;

entity vectormux2d is
    generic (B: INTEGER:= 8; -- bitwidth of each input
             N: INTEGER:= 16); -- number of inputs
    port (D: in std_logic_2d (N-1 downto 0, B-1 downto 0);
          sel: in std_logic_vector (ceil_log2(N)-1 downto 0);
          F: out std_logic_vector (B-1 downto 0));
end vectormux2d;

 architecture structure of vectormux2d is
    type chunk is array (N-1 downto 0) of std_logic_vector (B-1 downto 0);
    signal Di: chunk;
begin
    -- Converting std_logic_2d to chunk:
    st: for i in 0 to N-1 generate
        sk: for j in 0 to B-1 generate
            Di(i)(j) <= D(i,j);
        end generate;
    end generate;
    F <= Di(conv_integer(unsigned(sel)));
end structure;
```



- **vectormux2d.zip:**  
vectormux2d.vhd,  
tb\_vectormux2d.vhd  
pack\_xtras.vhd

# ✓ Custom arrays and packages




- **Example: Barrel shifter:** It uses: custom arrays X\_l, X\_r ( $N$  N-bit vectors), and the ceil\_log2() function defined in pack\_xtras.vhd.
- Parameters:  $N$ , SHIFTTYPE: ARITHMETIC, LOGICAL, ROTATION.
- Ports: idata/odata [ $N-1 \dots 0$ ], dir (shift direction), dist: # of bits to shift.

```
entity mybarrelshift is
    generic (N: integer:= 8;
              SHIFTTYPE: string:= "ARITHMETIC"); -- "ARITHMETIC", "LOGICAL", "ROTATION"
    port ( idata: in std_logic_vector (N-1 downto 0);
           dist: in std_logic_vector (ceil_log2(N) - 1 downto 0); -- dist: 0 to N-1
           dir: in std_logic; -- dir=1 -> RIGHT, dir =0: LEFT
           odata: out std_logic_vector (N-1 downto 0));
end mybarrelshift;
```


$N = 8$

dir	dist[2..0]	data[7..0]	result[7..0]		
			ARITHMETIC	LOGICAL	ROTATION
0	0 0 0	abcdefgh	abcdefgh	abcdefgh	abcdefgh
0	0 0 1	abcdefgh	bcdefgh0	bcdefgh0	bcdefgha
0	0 1 0	abcdefgh	cdefgh00	cdefgh00	cdefghab
0	0 1 1	abcdefgh	defgh000	defgh000	defghabc
0	1 0 0	abcdefgh	efgh0000	efgh0000	efghabcd
0	1 0 1	abcdefgh	fgh00000	fgh00000	fghabcde
0	1 1 0	abcdefgh	gh000000	gh000000	ghabcdef
0	1 1 1	abcdefgh	h0000000	h0000000	habcdgfg
1	0 0 0	abcdefgh	abcdefgh	abcdefgh	abcdefgh
1	0 0 1	abcdefgh	aabcdefg	0abcdefg	habcdgfg
1	0 1 0	abcdefgh	aaabedef	00abcdef	ghabcdef
1	0 1 1	abcdefgh	aaaabcde	000abcde	fghabcde
1	1 0 0	abcdefgh	aaaaabcd	0000abcd	efghabcd
1	1 0 1	abcdefgh	aaaaaaabc	00000abc	defghabc
1	1 1 0	abcdefgh	aaaaaaaaab	000000ab	cdefghab
1	1 1 1	abcdefgh	aaaaaaaaaa	0000000a	bcdefgha

 

- **mybarrelshift.zip:**  
 mybarrelshift.vhd,  
 tb\_mybarrelshift.vhd  
 pack\_xtras.vhd

# ✓ Example: Convolution Kernel

 

- This example uses parameterization (if-generate, for-generate) custom arrays, 2D vector arrays.



Convolution Size:  $N \times N$

Parameters:  $N, B, C, REP$  (unsigned/signed).

Ports:  $Di, Hi, F$ .  $Di: std\_logic\_2d$  of size  $N^2 \times B$ ,  $Hi: std\_logic\_2d$  of size  $N^2 \times C$ .

I/O Delay:  $\lceil \log_2 N^2 \rceil + 2$  clock cycles

  - Components: an input register array, an array of multipliers, and an adder tree.
- The figure shows a  $3 \times 3$  ( $N=3$ ) case:
- For easier manipulation,  $Di, Hi$  are turned into 2D vector arrays:



➤ **myconv2.zip:**  
 myconv2.vhd, my\_rege.vhd,  
 dffe.vhd, adder\_tree.vhd,  
 my\_addsub.vhd, fulladd.vhd  
 tb\_myconv2.vhd  
 pack\_xtras.vhd