

DIGITAL LOGIC WITH VHDL

(Fall 2013)

Unit 2

- *Use of std_logic_vector.*
- ✓ *CONCURRENT DESCRIPTION*
 - *‘with-select’, ‘when-else’ statements*
 - *Examples: multiplexor, decoder.*

✓ std_logic_vector

- In the example, we use the `std_logic_vector` type for an input signal.

```
library ieee;  
use ieee.std_logic_1164.all;
```


```
entity test is  
  port ( A: in std_logic_vector (3 downto 0);  
        -- A: |A3|A2|A1|A0|  
        y: out std_logic);  
end test;
```

```
architecture struct of test is
```

```
begin
```

```
-- The circuit represents an AND gate  
-- with 4 inputs: A(3), A(2), A(1), A(0)  
y <= A(3) and A(2) and A(1) and A(0);
```

```
end struct;
```

 

✓ std_logic_vector

- In the example, we use the `std_logic_vector` type for an output signal.

```
library ieee;
use ieee.std_logic_1164.all;


entity tst is
  port ( A,B: in std_logic;
        F: out std_logic_vector (3 downto 0);
        -- F: |F3|F2|F1|F0
  end tst;
```

architecture struct of tst is

begin

```
F(0) <= A and B; F(1) <= A xor B;
F(2) <= A or B; F(3) <= not(A);
```

end struct;

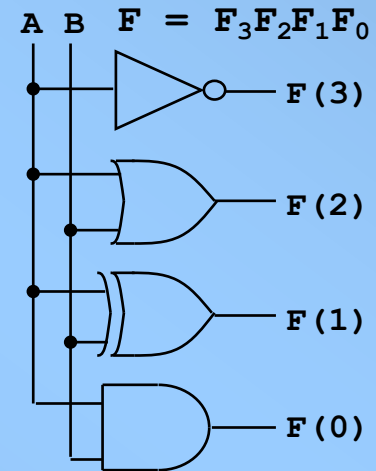


✓ *CONCURRENT DESCRIPTION*

- In this description, circuits are specified in an structured fashion. The order of the statements is irrelevant: all the statements represent circuits that are working at the same time. This type of description is well-suited for combinatorial circuits.
- The use of sentences with ‘and’, ‘or’, ‘xor’, ‘nand’, ‘nor’, ‘xnor’, and ‘not’ is a basic instance of the concurrent description. It is sometimes called ‘horizontal description’.
- In Unit 4, the so-called ‘structural description’ is just a generalization of the concurrent description.
- Since we already know how to build circuits based on logic gates, we now present two concurrent assignment statements (*with - select, when - else*), which are far more powerful than the statements with logic gates when it comes to describe complex circuits.

■ **CONCURRENT ASSIGNMENT STATEMENTS:**

 - **Selected Signal Assignment: WITH-SELECT:** This statement allows assigning values to a signal based on certain criterion.
- **MUX 2-to-1:**



$$y = \bar{s}(a \bar{b} + a b) + s(\bar{a} b + a b)$$

$$y = \bar{s}a + sb$$

with s select: 's' specifies the selection criterion
 when specifies the value assigned to 'y' for each value of 's'
 when others: we need to include all the possible values of 's', that are 9 according to *std_logic* type.

```

library ieee;
use ieee.std_logic_1164.all;

entity my_mux21 is
  port ( a, b, s: in std_logic;
         y: out std_logic);
end my_mux21;
  
```

```

architecture st of my_mux21 is
begin
  with s select
    y <= a when '0',
         b when others;
end st;
  
```

Selected Signal Assignment (WITH - SELECT):

MUX 8-to-1

```
library ieee;  
use ieee.std_logic_1164.all;
```


```
entity my_mux81 is  
  port ( a,b,c,d,e,f,g,h: in std_logic;  
        s: in std_logic_vector (2 downto 0);  
        y: out std_logic);  
end my_mux81;
```

```
architecture struct of my_mux81 is  
begin
```


```
  with s select
```

```
    y <= a when "000", -- note ',' instead of ';'!  
        b when "001",  
        c when "010",  
        d when "011",  
        e when "100",  
        f when "101",  
        g when "110",  
        h when others;
```

```
end struct;
```

 

 - Selected Signal Assignment(WITH - SELECT):
- MUX 6-to-1



```

library ieee;
use ieee.std_logic_1164.all;

entity my_mux61 is
  port ( a,b,c,d,e,f: in std_logic;
        s: in std_logic_vector (2 downto 0);
        y: out std_logic);
end my_mux61;

```

```

architecture struct of my_mux61 is
begin
  with s select
    y <= a when "000",
         b when "001",
         c when "010",
         d when "011",
         e when "100",
         f when "101",
         '- ' when others;
end struct;

```

Value '-': Don't care output
 It helps the synthesizer to optimize the circuit

← '- ' when others;

7-segment DECODER (outputs \geq inputs)

```


library ieee;
use ieee.std_logic_1164.all;

entity sevensseg is
  port ( bcd: in std_logic_vector (3 downto 0);
        sevensseg: out std_logic_vector (6 downto 0);
        EN: in std_logic_vector (3 downto 0));
end sevensseg;

architecture struct of sevensseg is
  signal leds: std_logic_vector (6 downto 0);
begin
  -- | a | b | c | d | e | f | g |
  -- |leds6|leds5|leds4|leds3|leds2|leds1|leds0|
  with bcd select
    leds <= "1111110" when "0000",
           "0110000" when "0001",
           "1101101" when "0010",
           "1111001" when "0011",
           "0110011" when "0100",
           "1011011" when "0101",
           "1011111" when "0110",
           "1110000" when "0111",
           "1111111" when "1000",
           "1111011" when "1001",
           "-----" when others;

  -- Nexys3: LEDs are active low.
  -- Each 7-seg display has an active-low enable
  EN <= "0111";
  sevensseg <= not(leds);
end struct;

```

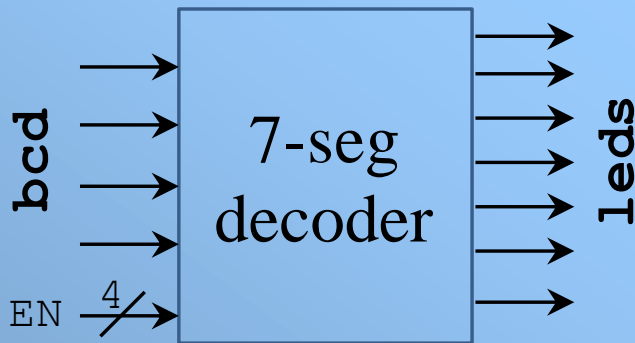


- Decoder 2-to-4 with enable:

```
library ieee;
use ieee.std_logic_1164.all;

entity dec2to4 is
  port (w: in std_logic_vector (1 downto 0);
        E: in std_logic;
        y: out std_logic_vector (3 downto 0));
end dec2to4;

 
architecture struct of dec2to4 is
  signal Ew: std_logic_vector (2 downto 0);
begin
  Ew <= E & w; -- concatenation
  with Ew select
    y <= "0001" when "100",
         "0010" when "101",
         "0100" when "110",
         "1000" when "111",
         "0000" when others;
end struct;
```



CONCURRENT ASSIGNMENT STATEMENTS :

- **Conditional signal assignment: WHEN - ELSE:** Similarly to the selected signal assignment, this statement allows a signal to take one out of many values based on a certain condition. The syntax however is different and it allows to describe circuits in a more compact fashion.

- **Example: MUX 2-to-1**

 


```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity mux21_cond is  
    port ( a, b, s: in std_logic;  
          y: out std_logic);  
end mux21_cond;
```

```
architecture est of mux21_cond is  
begin  
    y <= a when s = '0' else b;  
end est;
```

- If the condition on **when** is FALSE, we assign a value to 'y' after **else**. This assignment can also be conditioned by another **when-else** clause (see next example)

 - Conditional signal assignment (WHEN - ELSE):
- Example: MUX 4-to-1



- Note that the assignment on 'b' is conditioned by another **when-else** clause. Same for 'c'. Only the assignment of 'd' is not conditioned. There is no limit to the number of nested conditions.

```


library ieee;
use ieee.std_logic_1164.all;

entity mux41_cond is
  port (a, b, c, d: in std_logic;
        s: in std_logic_vector (1 downto 0);
        y: out std_logic);
end mux41_cond;

architecture est of mux41_cond is
begin
  y <= a when s = "00" else
      b when s = "01" else
      c when s = "10" else
      d;
end est;

```

 - Conditional signal assignment (WHEN - ELSE):
- Example: Priority Encoder 4-to-2



w ₃	w ₂	w ₁	w ₀	y ₁	y ₀	z
0	0	0	0	0	0	0
1	x	x	x	1	1	1
0	1	x	x	1	0	1
0	0	1	x	0	1	1
0	0	0	1	0	0	1

when-else has a priority level, thus it is easy to describe a priority encoder. With with-select describing this circuit would be very tedious.

```


library ieee;
use ieee.std_logic_1164.all;

entity my_prienc is
    port ( w: in std_logic_vector (3 downto 0);
          y: out std_logic_vector (1 downto 0);
          z: out std_logic);
end my_prienc;

architecture struct of my_prienc is
begin
    y <= "11" when w(3) = '1' else
        "10" when w(2) = '1' else
        "01" when w(1) = '1' else
        "00";
    z <= '0' when w = "0000" else '1';
    -- If no input is '1', z is '0'
end struct;

```

 - Conditional signal assignment (WHEN - ELSE):
- Example: 4-bit comparator



- Note the use of the operators '=', '>', '<' to compare numbers
- Always indicate what type of numbers we are working with. In the example we are using unsigned numbers. For 2's complement, use 'signed'.

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all; -- unsigned #s

entity my_comp is
  port ( A,B: in std_logic_vector (3 downto 0);
        AeqB, AgB, AlB: out std_logic);
end my_comp;

architecture struct of my_comp is
begin


  AeqB <= '1' when A = B else '0';
  AgB   <= '1' when A > B else '0';
  AlB   <= '1' when A < B else '0';

end struct;

```

- Conditional Signal Assignment (WHEN - ELSE):
- Example: Demultiplexor
 
```
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.std_logic_unsigned.all;
```



```
entity my_demux is  
  port ( s: in std_logic_vector (1 downto 0);  
         x: in std_logic;  
         a,b,c,d: out std_logic);  
end my_demux;
```

```
architecture struct of my_demux is  
begin
```

```
  a <= x when s = "00" else '0';  
  b <= x when s = "01" else '0';  
  c <= x when s = "10" else '0';  
  d <= x when s = "11" else '0';
```

```
end struct;
```