

Homework 1

(Due date: September 12th @ 9:30 am)
Presentation and clarity are very important!

PROBLEM 1 (15 PTS)

a) Simplify the following functions using ONLY Boolean Algebra Postulates and Theorems. For each resulting simplified function, sketch the logic circuit using AND, OR, XOR, and NOT gates.

✓ $F = A(C + \bar{B}) + \bar{A}$

✓ $F = (Y + Z)(\bar{Y} + X)$

✓ $F(X, Y, Z) = \prod(M_0, M_1, M_4, M_5)$

✓ $F = \overline{(X + Y)Z} + X\bar{Y}Z$


b) For the following Truth table with two outputs:

- Provide the Boolean functions using: Sum of Products (SOP), and Product of Sums (POS).
- Express the Boolean functions using the minterms and maxterms representations.
- Sketch the logic circuits.

x	y	z	f ₁	f ₂
0	0	0	0	0
0	0	1	1	1
0	1	0	0	1
0	1	1	1	1
1	0	0	1	0
1	0	1	0	1
1	1	0	1	0
1	1	1	1	1

PROBLEM 2 (15 PTS)

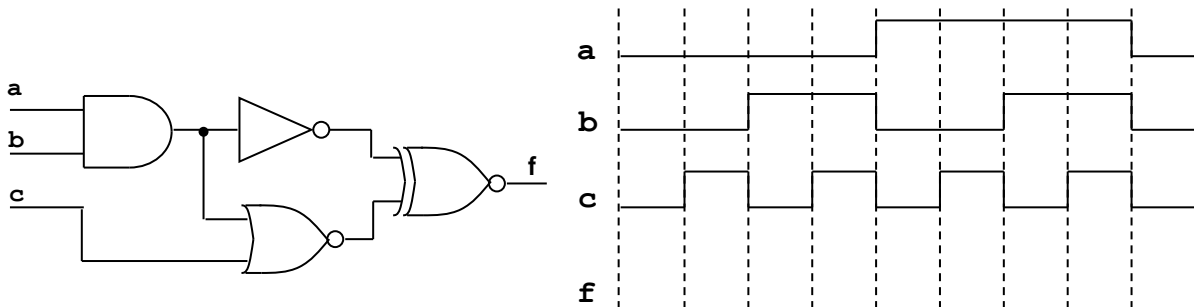a) Complete the timing diagram of the following circuit:




b) Complete the timing diagram of the logic circuit whose VHDL description is shown below:

```

library ieee;
use ieee.std_logic_1164.all;

entity circ is
  port ( a, b, c: in std_logic;
        f: out std_logic);
end circ;

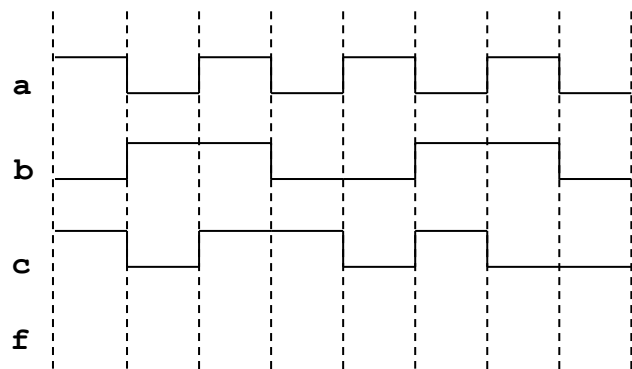architecture st of circ is
  signal x, y: std_logic;
begin
  x <= a and b;
  y <= x nand c;
  f <= y xor (not b);
end st;
    
```



- c) The following is the timing diagram of a logic circuit with 3 inputs. Sketch the logic circuit that generates this waveform. Then, complete the VHDL code.

```


library ieee;
use ieee.std_logic_1164.all;

entity circ is
  port ( a, b, c: in std_logic;
        f: out std_logic);
end circ;

architecture st of circ is
-- ???
begin
-- ???


end st;

```

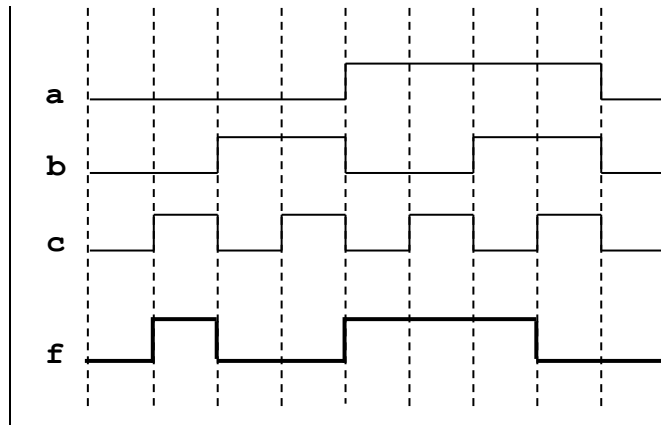

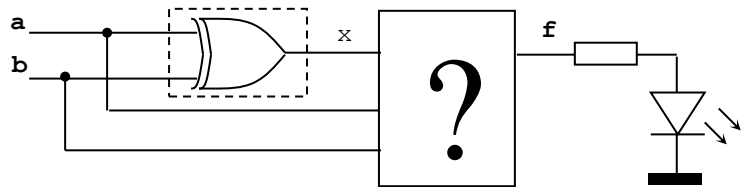PROBLEM 3 (15 PTS)


Design a circuit (simplify your circuit) that verifies the logical operation of a XOR gate. $f = '1'$ (LED ON) if the XOR gate does NOT work properly. Assumption: when the XOR gate is not working, it generates 1's instead of 0's and vice versa.



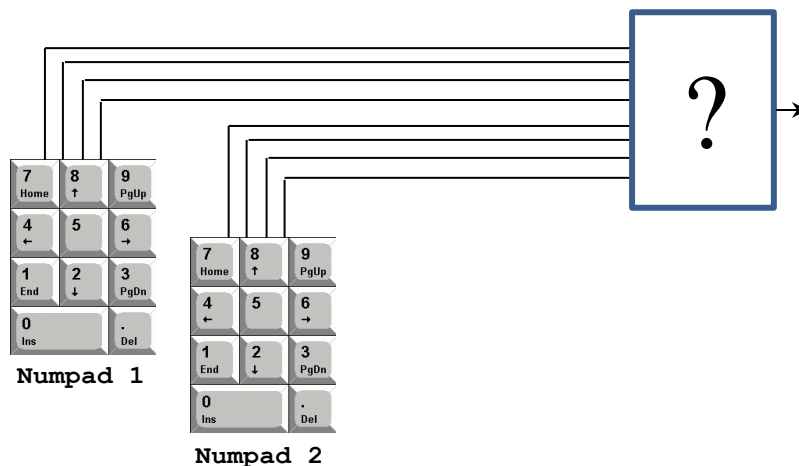PROBLEM 4 (10 PTS)

Design a logic circuit (simplify your circuit) that opens a lock ($f = '1'$) whenever one presses the correct number on each numpad. We encode each decimal number on the numpad using BCD encoding. We expect that each group of 4 bits be in the range from 0000 to 1001, the values from 1010 to 1111 are assumed not to occur.

- Tip: create two circuits: one that verifies the first number (9), and the other that verifies the second number (5). Then perform the AND operation on the two outputs. This avoids creating a truth table with 8 inputs!






PROBLEM 5 (20 PTS)

We want to display the hexadecimal value of a 4-bit number on a 7-segment display. The LEDs are lit with a logical '0' (negative logic or active low). The inputs are active high (or in positive logic).

- Complete the truth table for each output (a-g).
- Provide the simplified expression for each output (a-g)

b_3	b_2	b_1	b_0	a	b	c	d	e	f	g
0	0	0	0							
0	0	0	1							
0	0	1	0							
0	0	1	1							
0	1	0	0							
0	1	0	1							
0	1	1	0							
0	1	1	1							
1	0	0	0							
1	0	0	1	0	0	0	0	1	0	0
1	0	1	0							
1	0	1	1							
1	1	0	0							
1	1	0	1							
1	1	1	0	0	1	1	0	0	0	0
1	1	1	1							

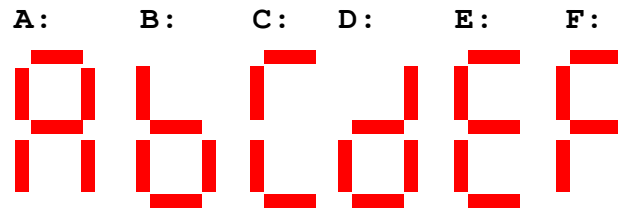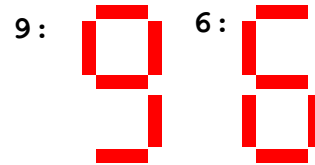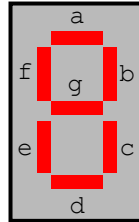

PROBLEM 6 (25 PTS)

In these problems, you MUST show your conversion procedure.

- Convert the following decimal numbers to i) binary, ii) octal, and iii) hexadecimal.
 - 124, 200, 115, 128, 511.25, 64.625, 19.6875.
- What is the minimum number of bits required to represent:
 - 50,000 colors?
 - 32679 symbols?
 - Numbers between 25,000 and 29,095?
 - 65536 memory addresses in a computer?
- A microprocessor can handle addresses from 0x0000 to 0x7FFF. How many bits do we need to represent those addresses?
- Complete the following table.

Decimal	BCD	Binary number	Reflective Gray Code
		1010100110	
			1011100010
128			
		10101011	
	01001001		
			10001001
		1110010	
			110011101
442			
	011000110001		