

# Homework 2

(Due date: October 3rd @ 9:30 am)  
Presentation and clarity are very important!

## PROBLEM 1 (10 PTS)

- Complete the following table. Use the fewest number of bits for every case. Show your procedure.

Decimal	Sign-and-magnitude	1's complement	2's complement
-257			
128			
-120			
-61			
-1022			
511			

## PROBLEM 2 (15 PTS)

- We need to perform the following operations, where numbers are represented in 2's complement:
  - $73 + 45$
  - $-35 + 64$
  - $-129 + 128$
  - $-255 - 230$
  - $490 + 47$
  - $990 + 113$
- For each case:
  - ✓ Determine the minimum number of bits required to represent both summands. You might need to sign-extend one of the summands, since for proper summation, both summands must have the same number of bits.
  - ✓ Perform the binary addition in 2's complement arithmetic. The result must have the same number of bits as the summands.
  - ✓ Determine whether there is overflow by:
    - Using  $c_n, c_{n-1}$  (carries).
    - Performing the operation in the decimal system and checking whether the result is within the allowed range for  $n$  bits, where  $n$  is the minimum number of bits for the summands.
  - ✓ If we want to avoid overflow, what is the minimum number of bits required to represent the summands and the result?

## PROBLEM 3 (15 PTS)

- Sign-extension in 2's complement: Whenever we need to increase the number of bits for representing a number, we append the MSB to the left as many times as needed:

$$b_{n-1}b_{n-2} \dots b_0 \equiv b_{n-1} \dots b_{n-1}b_{n-1}b_{n-2} \dots b_0$$

Examples:  $00101_2 = 0000101_2 = 2^2 + 2^0 = 5$   
 $10101_2 = 1110101_2 = -2^4 + 2^2 + 2^0 = -2^6 + 2^5 + 2^4 + 2^2 + 2^0 = -11$

We can think of the sign-extended number as an  $m$ -bit number, where  $m > n$ :

$$b_{n-1} \dots b_{n-1}b_{n-1}b_{n-2} \dots b_0 = k_{m-1} \dots k_n k_{n-1} k_{n-2} \dots k_0$$

- Demonstrate that  $b_{n-1}b_{n-2} \dots b_0$  represents the same decimal number as  $b_{n-1} \dots b_{n-1}b_{n-1}b_{n-2} \dots b_0$ , i.e., demonstrate that sign-extension is correct for any  $m > n$ .


Useful formula:  $\sum_{i=k}^l r^i = \frac{r^{k-r^{l+1}}}{1-r}, r \neq 1$

## PROBLEM 4 (15 PTS)

- Implement the following functions using i) decoders and ii) multiplexers:
  - ✓  $F = \overline{X} + \overline{Z} + YZ$
  - ✓  $F(X, Y, Z) = \prod(M_1, M_4, M_7)$
  - ✓  $F = XY + YZ + XZ$
  - ✓  $F = X \oplus Y \oplus Z$
- Using only 2-to-1 MUXs, implement the XOR and XNOR gates.
- Using only a 4-to-1 MUX, implement the following functions.
  - $F(X, Y, Z) = \sum(m_1, m_3, m_5, m_7)$
  - $F(X, Y, Z) = \sum(m_3, m_5, m_7)$
  - $F(X, Y, Z) = \sum(m_1, m_3, m_5)$
  - $F(X, Y, Z) = \sum(m_5, m_7)$

 
PROBLEM 5 (10 PTS)

- A 20-bit address line in a  $\mu$ processor handles up to  $2^{20} = 1\text{ MB}$  of addresses, each address containing one-byte of information. We want to connect four 256KB memory chips to the  $\mu$ processor.
- Sketch the circuit that: i) addresses the memory chips, and ii) enables only one memory chip (via CE: chip enable) when the address falls in the corresponding range. Example: if  $address = 0x5FFFF$ ,  $\rightarrow$  only memory chip 2 is enabled ( $CE=1$ ). If  $address = 0xD0123$ ,  $\rightarrow$  only memory chip 4 is enabled.




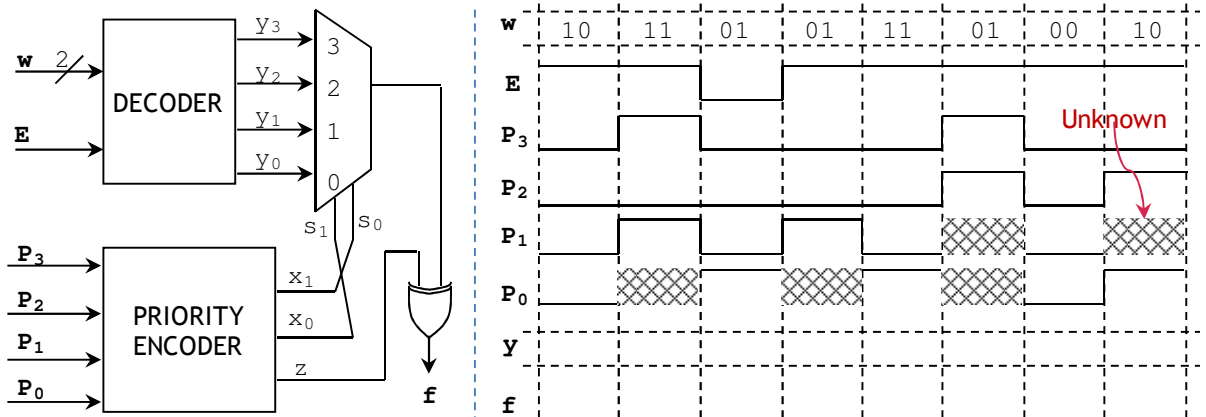PROBLEM 6 (15 PTS)

- Complete the timing diagram of the circuit shown below:



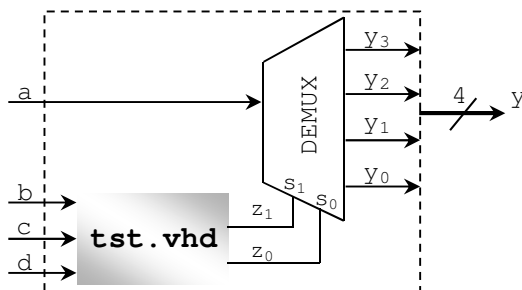- The following VHDL code corresponds to the shaded circuit. Complete the timing diagram:




```

library ieee;
use ieee.std_logic_1164.all;

entity tst is
  port (b,c,d: in std_logic;
        z: out std_logic_vector(1 downto 0));
end tst;
    
```


```

 architecture bhv of circ is
  signal x, y: std_logic;
begin
  process (b,c,d)
  begin
    z <= c & d;
    if b = '1' then
      case d is
        when '1' => z <= "01";
        when others => z <= "00";
      end case;
    else
      if c = '0' then z <= "11";
      end if;
    end if;
  end process;
end bhv;
    
```






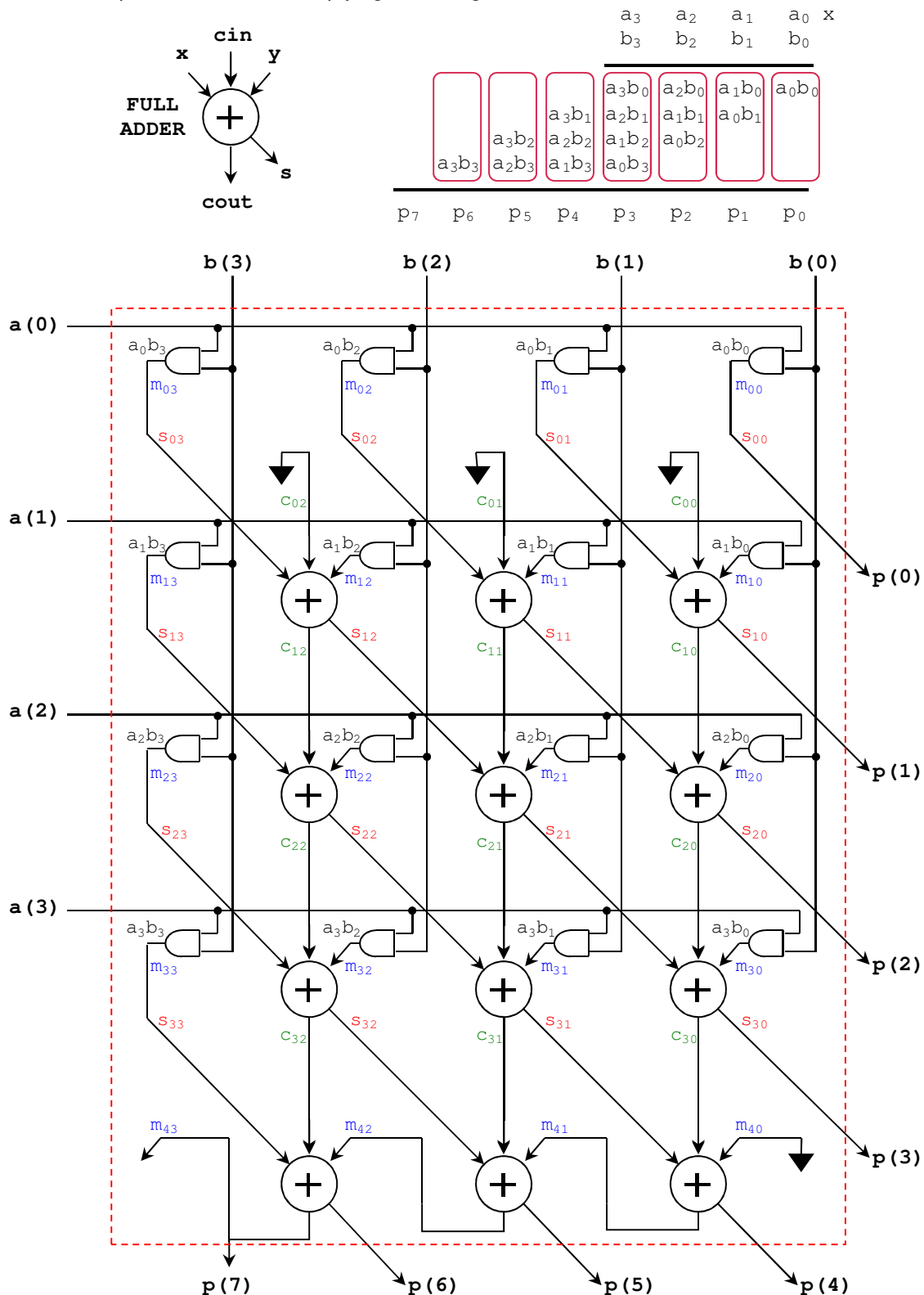
PROBLEM 7 (20 PTS)

- A straightforward implementation of the multiplication operation (for positive or unsigned numbers) is called **Array Multiplier**: the partial products are added up at every column. The figure depicts the hardware implementation for multiplying two unsigned number of 4 bits.



- One of the drawbacks of this approach is the long delay between the input and the output. In the figure, the bits  $p_7, p_6, p_5, p_4$  require the inputs to pass through 4 adders as well as AND gates.

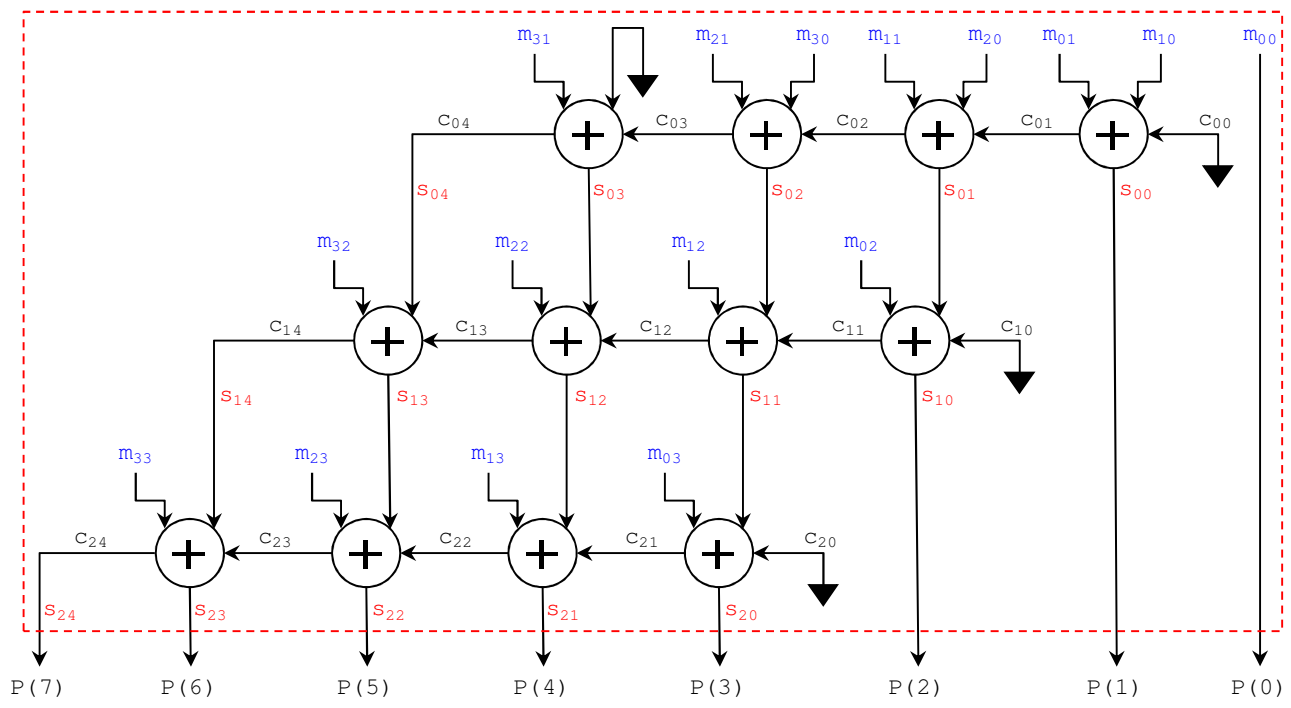  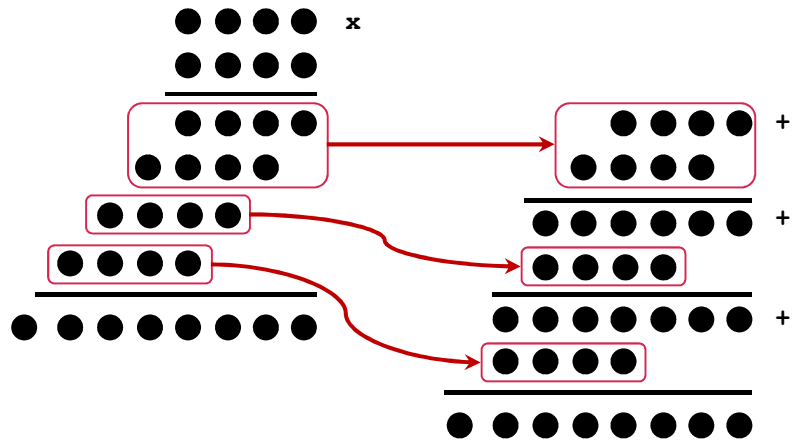- An alternative implementation, called **Wallace Multiplier**, features a shorter delay between the input and the output. The hardware implementation is more complicated though.
- The figure shows a Wallace multiplier implementation for two unsigned numbers of 4 bits. Note how the addition operation of the 4 rows has been rearranged so that only 2 rows are added up at every stage.



- ✓ Write the VHDL implementation for the multiplication operation of two unsigned numbers of 4 bits using: i) Array Multiplier, and ii) Wallace multiplier. Use the **Structural Description**: create a separate VHDL file for the Full Adder circuit.
- ✓ Simulate both circuits and make sure that they are performing the correct operation.
- ✓ Attach your VHDL code, testbench code, and simulation results.