

# Solutions - Quiz 2

(October 3rd @ 9:30 am)



## PROBLEM 1 (20 PTS)

- Implement the following functions using i) decoders (and gates) and ii) multiplexers:

✓  $F_a(X, Y, Z) = \overline{X} + \overline{Y} + Z$

✓  $F_b(X, Y, Z) = \prod(M_3, M_4, M_7)$

	w <sub>2</sub>	w <sub>1</sub>	w <sub>0</sub>		
	x	y	z	F <sub>a</sub>	F <sub>b</sub>
	0	0	0	1	1
	0	0	1	1	1
	0	1	0	0	1
	0	1	1	1	0
	1	0	0	0	0
	1	0	1	1	1
	1	1	0	0	1
	1	1	1	1	0

  

## PROBLEM 2 (20 PTS)


- Complete the timing diagram of the circuit whose VHDL description is shown below:

```
library ieee;
use ieee.std_logic_1164.all;

entity tst is
    port (a,b,c: in std_logic;
          z: out std_logic_vector(1 downto 0));
end tst;

architecture bhv of tst is
```
 
```
begin
    process (a,b,c)
    begin
        z <= a & c;
        if b = '1' then
            z <= "01";
        end if;
    end process;
end bhv;
```



PROBLEM 3 (30 PTS)

- Perform the following operations using the 2's complement representation. For each case, provide the summands and the result in 2's complement representation. Use the minimum number of bits to represent the summands and the result so that overflow is avoided.
  - ✓  $-17 + 32$
  - ✓  $-127 - 31$

**n = 7 bits**

$$\begin{array}{r} \overline{\overline{c_7}} \overline{\overline{c_6}} \\ -17 = 1101111 + \\ +32 = 0100000 \\ \hline +15 = 0001111 \\ \text{overflow} = c_7 \oplus c_6 = 0 \rightarrow \text{no overflow} \\ +15 \in [-2^6, 2^6-1] \rightarrow \text{no overflow} \end{array}$$

**n = 8 bits**

$$\begin{array}{r} \overline{\overline{c_8}} \overline{\overline{c_7}} \\ -127 = 10000001 + \\ -31 = 11100001 \\ \hline 01100010 \\ \text{overflow} = c_8 \oplus c_7 = 1 \rightarrow \text{overflow!} \\ -127 - 31 = -158 \notin [-2^7, 2^7-1] \rightarrow \text{overflow!} \end{array}$$

**To avoid overflow:**

**n = 9 bits (sign-extension):**

$$\begin{array}{r} \overline{\overline{c_9}} \overline{\overline{c_8}} \\ -127 = 110000001 + \\ -31 = 111100001 \\ \hline -158 = 101100010 \\ \text{overflow} = c_9 \oplus c_8 = 0 \rightarrow \text{no overflow} \\ -158 \in [-2^8, 2^8-1] \rightarrow \text{no overflow} \end{array}$$

PROBLEM 4 (30 PTS)

- Complete the timing diagram of the circuit shown below:

