



Solutions - Quiz 3

(October 31st @ 9:30 am)



  PROBLEM 1 (20 PTS)

- Complete the timing diagram of the following state machine:




PROBLEM 2 (25 PTS)

- Complete the timing diagram of the circuit whose VHDL description is shown below:

```
library ieee;
use ieee.std_logic_1164.all;


entity circ is
    port ( rstn, a,b, x, clk: in std_logic;
          q: out std_logic);
end circ;
```
 
```
architecture hallows of circ is
    signal qt: std_logic;
begin
    process (rstn, clk, a, b, x)
    begin
        if rstn = '0' then
            qt <= '0';
        elsif (clk'event and clk = '1') then
            if x = '1' then
                qt <= not(qt);
            else
                qt <= a and b;
            end if;
        end if;
    end process;
    q <= qt;
end hallows;
```



 PROBLEM 3 (25 PTS)

- Sequence detector (with overlap): Draw the state diagram of a circuit that detects the following sequence: 010011. The detector must assert an output 'z=1' when the sequence is detected.



PROBLEM 4 (30 PTS)

- Complete the timing diagram of the following circuit. $Q = Q_3Q_2Q_1Q_0$

