

DIGITAL LOGIC WITH VHDL

(Fall 2013)

Unit 4

✓ *'Integer' DATA TYPE*

✓ *STRUCTURAL DESCRIPTION*

- Hierarchical design: port-map, for-generate, if-generate.
- Examples: Adders, comparators, multipliers, Look-up Tables, Barrel shifter

✓ *INTEGER* Data Type

- A signal of type ‘*integer*’ represents a binary number. But we do not specify the number of bits for the signal, only the range of decimal values (this can be very convenient).

- **Example:** 7-segment decoder. The BCD input is an integer from 0 to 9, requiring 4 bits (computed by the synthesizer).

- **Drawback:** the datatype ‘*integer*’ does not allow access to the individual bits (unlike ‘*std_logic_vector*’)


```
library ieee;
use ieee.std_logic_1164.all;

entity sevenseg is
    port ( bcd: in integer range 0 to 9;
          -- bcd: 0000 to 1001 -> 4 bits required
          sevenseg: out std_logic_vector (6 downto 0);
          EN: in std_logic_vector (3 downto 0));
end sevenseg;

architecture struct of sevenseg is
    signal leds: std_logic_vector (6 downto 0);
begin
    -- | a | b | c | d | e | f | g |
    -- |leds6|leds5|leds4|leds3|leds2|leds1|leds0|
    with bcd select
        leds <= "1111110" when 0,
               "0110000" when 1,
               "1101101" when 2,
               "1111001" when 3,
               "0110011" when 4,
               "1011011" when 5,
               "1011111" when 6,
               "1110000" when 7,
               "1111111" when 8,
               "1111011" when 9;
    -- Nexys3: LEDs are active low.
    -- Each 7-seg display has an active-low enable
    EN <= "0111";
    sevenseg <= not(leds);
end struct;
```

✓ *STRUCTURAL DESCRIPTION*

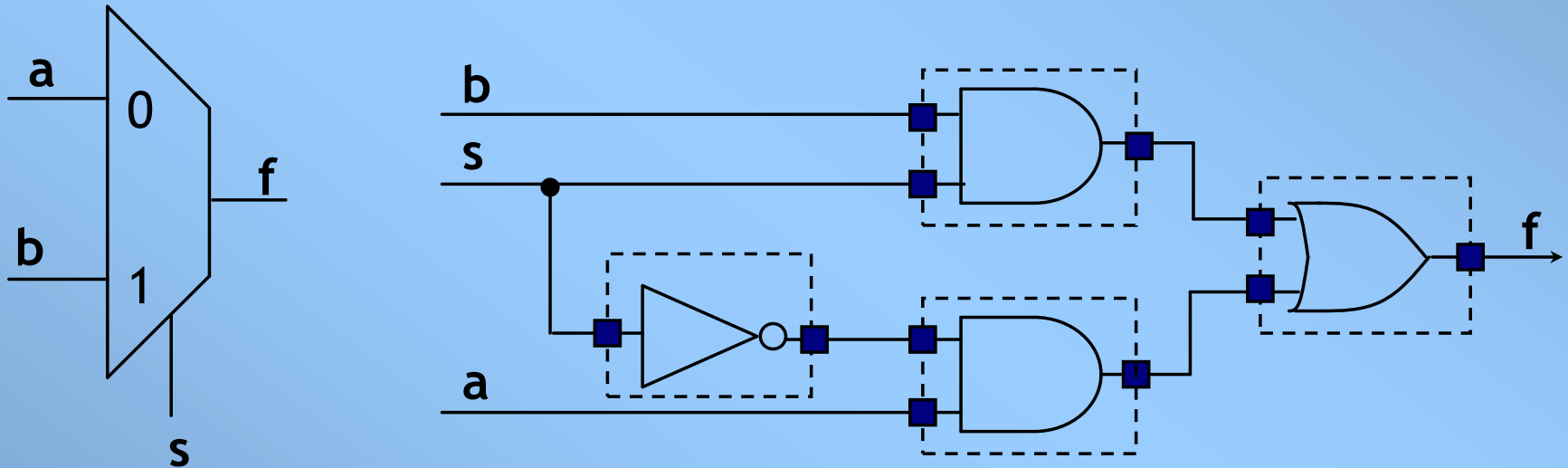- It is the generalization of the Concurrent Description. The circuits are described via interconnection of its subcircuits. This subcircuits can be described in concurrent code and/or sequential code.
- Example:** Multiplexor 2-to-1.




- This case is trivial, since the interconnection is realised via logic operators, but nevertheless it is an example of structural description.

✓ *STRUCTURAL DESCRIPTION*

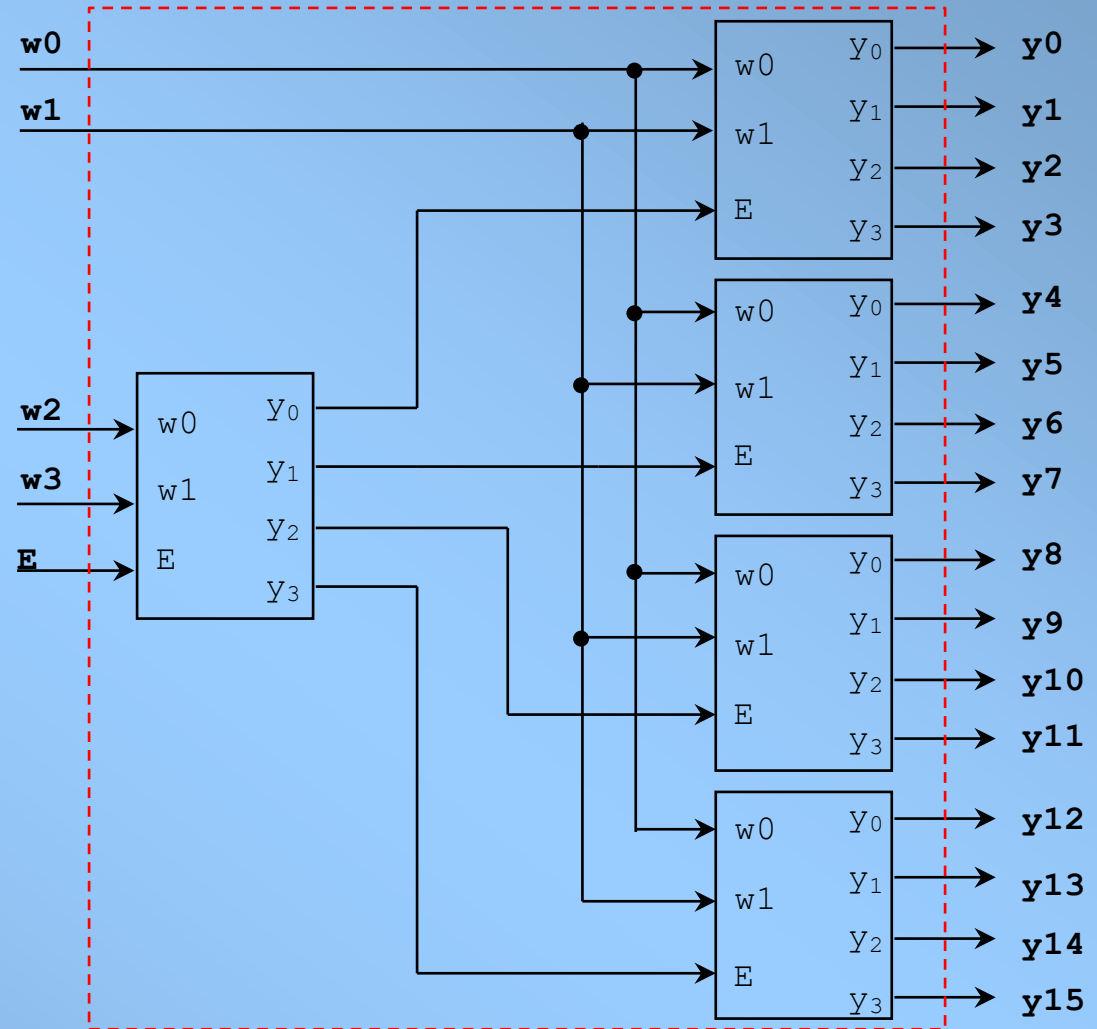- Example: 4-to-16 decoder


- We can describe this decoder in a structured way based on 2-to-4 decoders.

- However, we can also describe the 4-to-16 decoder using the with-select statement.



✓ *STRUCTURAL DESCRIPTION*

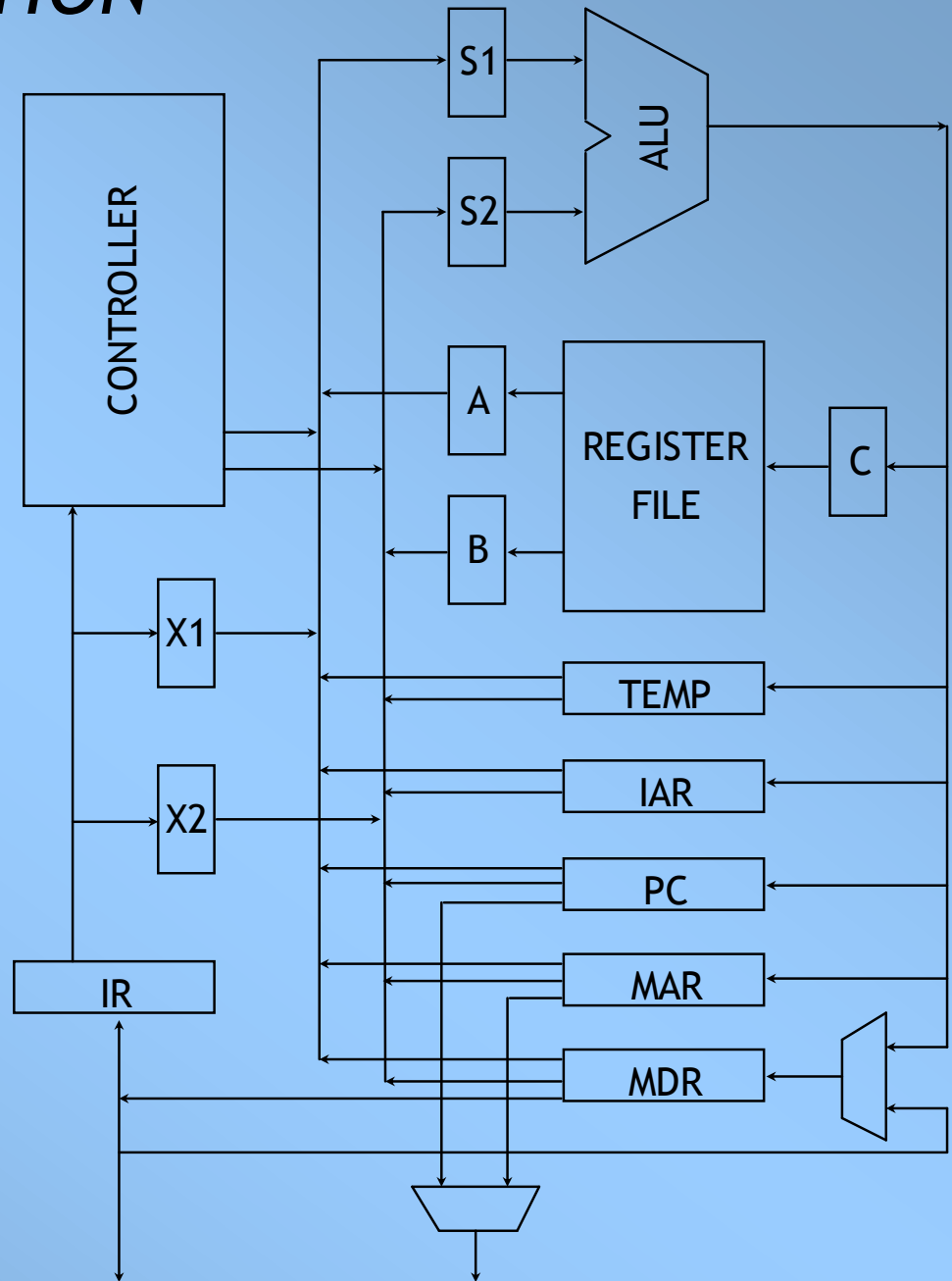- **Example: DLX Processor**
- In this type of systems, it is best to describe each component first, then assemble them to make the large system.
- We do not need to see such large system to realise the importance of the Structural Description.



✓ *STRUCTURAL DESCRIPTION*

- Many systems can be described entirely in one single block: we can use the behavioral description, and/or concurrent statements (with-select, when-else).
- However, it is advisable not to abuse of this technique since it makes: i) the code less readable, ii) the circuit verification process more cumbersome, and iii) circuits improvements less evident.
- The structural description allows for a hierarchical design: we can 'see' the entire circuit as the pieces it is made of, then identify critical points and/or propose improvements on each piece.
- It is always convenient to have basic building blocks from which we can build more complex circuits. This also allows building block (or sub-system) to be re-used in a different circuit.

✓ 4-bit 2's complement Adder

- Full Adder: VHDL Description (fulladd.vhd):


```
library ieee;  
use ieee.std_logic_1164.all;
```

```
entity fulladd is  
  port ( cin, x, y: in std_logic;  
        s, cout: out std_logic);  
end fulladd;
```

```
architecture struct of fulladd is  
begin
```

```
  s <= x xor y xor cin;  
  cout <= (x and y) or (x and cin) or (y and cin);
```

```
end struct;
```

 

✓ 4-bit 2's complement Adder

- Top file (my_addsub.vhd): We need 4 full adders block and extra logic circuitry.

```
library ieee;
use ieee.std_logic_1164.all;

entity my_addsub is
  port ( addsub: in std_logic;
        x,y: in std_logic_vector(3 downto 0);
        s: out std_logic_vector(3 downto 0);
        cout, overflow: out std_logic);
end my_addsub;

architecture struct of my_addsub is
  component fulladd
    port ( cin, x, y: in std_logic;
          s, cout: out std_logic);
  end component;

  signal c: out std_logic_vector(4 downto 0);
  signal yt: out std_logic_vector(3 downto 0);

begin -- continued on next page
```

In order to use the file 'fulladd.vhd' into the top file, we need to declare it in the top file:

We copy what is in the entity of full_add.vhd

✓ 4-bit 2's complement Adder

- Here, we:
 - Insert the required extra circuitry (xor gates and I/O connections).
 - Instantiate the full adders and interconnect them (using the `port map` statement)

-- continuation from previous page

```
c(0) <= addsub; cout <= c(4);  
overflow <= c(4) xor c(3);
```

```
yt(0) <= y(0) xor addsub; yt(1) <= y(1) xor addsub;  
yt(2) <= y(2) xor addsub; yt(3) <= y(3) xor addsub;
```

```
f0: fulladd port map(cin=>c(0), x=>x(0), y=>yt(0), s=>s(0), cout=>c(1));  
f1: fulladd port map(cin=>c(1), x=>x(1), y=>yt(1), s=>s(1), cout=>c(2));  
f2: fulladd port map(cin=>c(2), x=>x(2), y=>yt(2), s=>s(2), cout=>c(3));  
f3: fulladd port map(cin=>c(3), x=>x(3), y=>yt(3), s=>s(3), cout=>c(4));
```

```
end struct;
```


✓ 4-bit 2's complement Adder

- Use of 'port map' statement:

```
port map (signal in full adder => signal in top file, ...)
```

- Instantiating and connecting the first full adder:
 
```
f0: fulladd port map (cin=>c(0), x=>x(0), y=>yt(0), s=>s(0), cout=>c(1));
```




✓ 4-bit 2's complement Adder

- Use of 'port map' statement:

`port map (signal in full adder => signal in top file, ...)`

- Instantiating and connecting the second full adder:
 
```
f1: fulladd port map(cin=>c(1), x=>x(1), y=>yt(1), s=>s(1), cout=>c(2));
```




✓ 4-bit 2's complement Adder

- Use of 'port map' statement:

`port map (signal in full adder => signal in top file, ...)`

- Instantiating and connecting the third full adder:
 
```
f2: fulladd port map(cin=>c(2), x=>x(2), y=>yt(2), s=>s(2), cout=>c(3));
```




✓ 4-bit 2's complement Adder

- Use of 'port map' statement:

```
port map (signal in full adder => signal in top file, ...)
```

- Instantiating and connecting the fourth full adder:
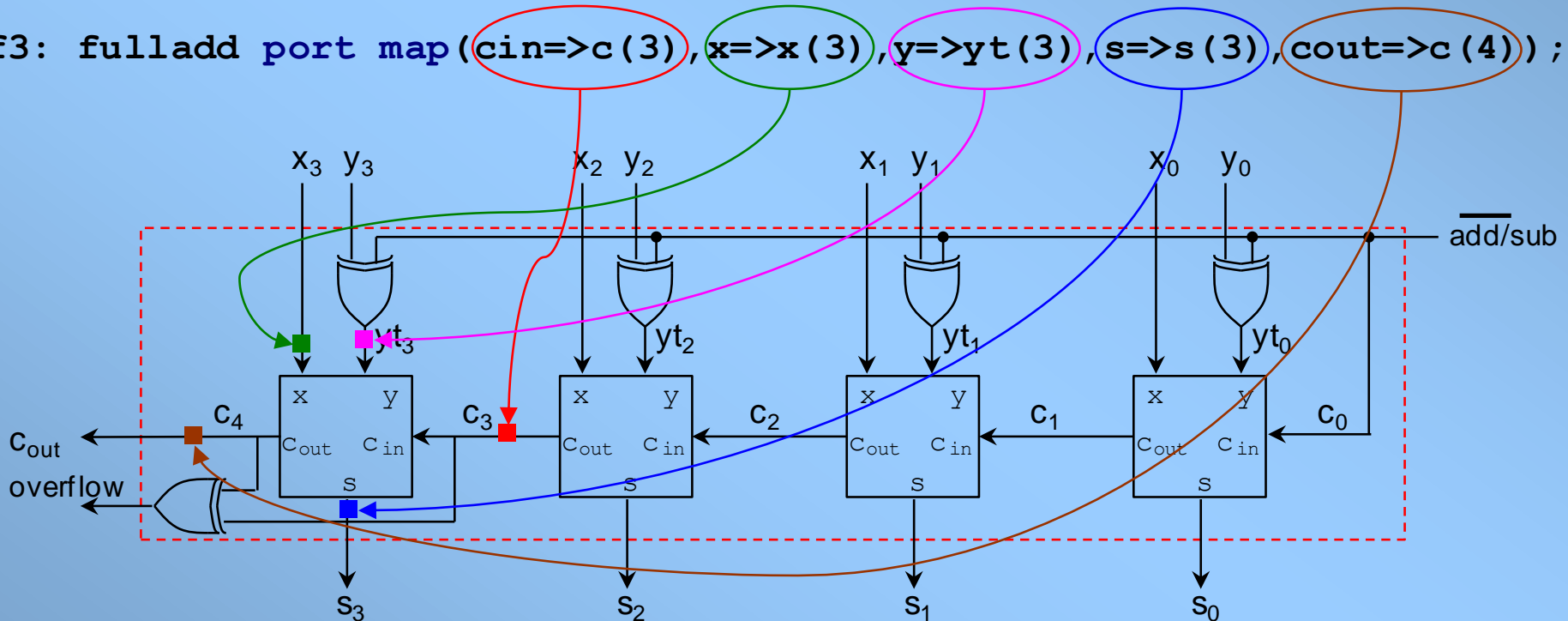
```
f3: fulladd port map(cin=>c(3), x=>x(3), y=>yt(3), s=>s(3), cout=>c(4));
```



✓ STRUCTURAL DESCRIPTION

- In the 4-bit adder example, if we wanted to use say 8 bits, we would need to instantiate 8 full adders and write 8 port map statements.
- **For-generate:** Instantiating components can be a repetitive task, thus the *for-generate* statement is of great help here:

```
yt(0) <= y(0) xor addsub; yt(1) <= y(1) xor addsub;  
yt(2) <= y(2) xor addsub; yt(3) <= y(3) xor addsub;
```

```
f0: fulladd port map (cin=>c(0), x=>x(0), y=>yt(0), s=>s(0), cout=>c(1));  
f1: fulladd port map (cin=>c(1), x=>x(1), y=>yt(1), s=>s(1), cout=>c(2));  
f2: fulladd port map (cin=>c(2), x=>x(2), y=>yt(2), s=>s(2), cout=>c(3));  
f3: fulladd port map (cin=>c(3), x=>x(3), y=>yt(3), s=>s(3), cout=>c(4));
```

-- continuation from previous page

```
c(0) <= addsub; cout <= c(4);  
overflow <= c(4) xor c(3);
```

```
gi: for i in 0 to 3 generate  
    yt(i) <= y(i) xor addsub;  
    fi: fulladd port map (cin=>c(i), x=>x(i), y=>yt(i), s=>s(i), cout=>c(i+1));  
end generate;  
end struct;
```