

# DIGITAL LOGIC WITH VHDL

## (Fall 2013)

### Unit 5


#### ✓ *SEQUENTIAL CIRCUITS*

- Asynchronous sequential circuits: Latches
- Synchronous circuits: flip flops, counters, registers.


# ✓ COMBINATORIAL CIRCUITS

- In combinatorial circuits, the output only depends upon the present input values.
- There exist another class of logic circuits whose outputs not only depend on the present input values but also on the past values of inputs, outputs, and/or internal signal. These circuits include storage elements to store those previous values.
- The content of those storage elements represents the *circuit state*. When the circuit inputs change, it can be that the circuit stays in certain state or changes to a different one. Over time, the circuit goes through a sequence of states as a result of a change in the inputs. The circuits with this behavior are called *sequential circuits*.

COMBINATORIAL CIRCUIT

 

SEQUENTIAL CIRCUIT

 


# ✓ *SEQUENTIAL CIRCUITS*

- Combinatorial circuits can be described with concurrent statement, or behavioral statements.
- Sequential circuits are *best described* with sequential statements.
- Sequential circuits can either be synchronous or asynchronous. In VHDL, they are described with asynchronous/synchronous processes.
- Basic asynchronous sequential circuit: Latch
- Basic synchronous sequential circuits: flip flops, counters, and registers.
  
- We will now go over the VHDL description of sequential circuits.
 
# ✓ ASYNCHRONOUS PROCESS (LATCHES)

- SR Latch
- An SR Latch based on NOR gates::





S	R	$Q_{t+1}$	$\overline{Q}_{t+1}$
0	0	$Q_t$	$\overline{Q}_t$
0	1	0	1
1	0	1	0
1	1	0	0

restricted

- According to its truth table, the output can be assigned to either '0' or '1'. This circuit state ('0' or '1') is stored in the circuit when  $S=R='0'$ .

▪ SR Latch:

  

```


library ieee;
use ieee.std_logic_1164.all;

entity latch_sr is
    port ( s,r: in std_logic;
          q, qn: out std_logic);
end latch_sr;

architecture bhv of latch_sr is
    signal qt,qnt: std_logic;
begin
    process (s,r)
    begin
        if s='1' and r='0' then
            qt<='1'; qnt<='0';
        elsif s='0' and r='1' then
            qt<='0'; qnt <='1';
        elsif s='1' and r='1' then
            qt<='0'; qnt <= '0';
        end if;
    end process;
    -- we don't specify what happens
    -- if s=r='0' --> q, qn kept their
    -- previous values
    q <= qt; qn <= qnt;
end bhv;

```

# SR Latch with enable

 

E	S	R	$Q_{t+1}$	$\overline{Q}_{t+1}$
0	x	x	$Q_t$	$\overline{Q_t}$
1	0	0	$Q_t$	$\overline{Q_t}$
1	0	1	0	1
1	1	0	1	0
1	1	1	0	0

■ Note: If E = '0', the previous output is kept.

```


library ieee;
use ieee.std_logic_1164.all;

entity latch_sr_E is
  port ( s,r, E: in std_logic;
         q, qn: out std_logic);
end latch_sr_E;

architecture bhv of latch_sr_E is
  signal qt,qnt: std_logic;
begin
  process (s,r)
  begin
    if E = '1' then
      if s='1' and r='0' then
        qt<='1'; qnt<='0';
      elsif s='0' and r='1' then
        qt<='0'; qnt <='1';
      elsif s='1' and r='1' then
        qt<='0'; qnt <= '0';
      end if;
    end if;
  end process;
  q <= qt; qn <= qnt;
end bhv;

```

▪ D Latch D with enable

 

E	D	$Q_{t+1}$
0	x	$Q_t$
1	0	0
1	1	1

```

library ieee;
use ieee.std_logic_1164.all;

entity latch_D is
    port ( D, E: in std_logic;
          q, qn: out std_logic);
end latch_D;


architecture bhv of latch_D is
    signal qt: std_logic;
begin
    process (D,E)
    begin
        if E = '1' then
            qt <= d;
        end if;
    end process;
    q <= qt; qn <= not(qt);
end bhv;

```

# ✓ SYNCHRONOUS PROCESSES
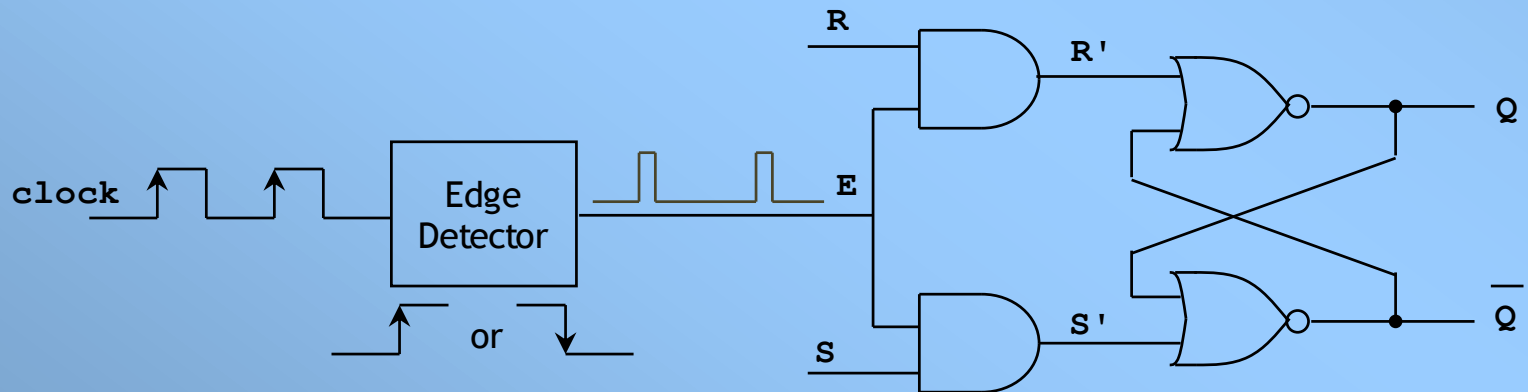
## ▪ Flip Flops



- Unlike a Latch, a flip flop only changes its outputs on the edge (rising or falling) of a signal called *clock*. A *clock* signal is an square wave with a fixed frequency.
- To detect a rising or falling edge, flip flops include an edge detector circuit. Input: a *clock* signal, Output: short duration pulses during the rising (or falling) clock edges. These pulses are then connected to the enable input in a Latch.
- For example, an SR flip flop is made out of: a SR Latch with an edge detector circuit. The edge detector generates enable signals during the during the rising (or falling) clock edges.





 
 
# ✓ SYNCHRONOUS PROCESSES

- **Flip Flops:** The edge detector circuit generates  $E=‘1’$  during the edge (rising or falling). We will work with circuits activated by either rising or falling edge. We will not work with circuits activated by both edges.
- An example of a circuit that detects a rising edge is shown below. The redundant NOT gates cause a delay that allows a pulse to be generated during a rising edge (or positive edge).




# ✓ SYNCHRONOUS PROCESSES

## ▪ SR Flip Flop

  

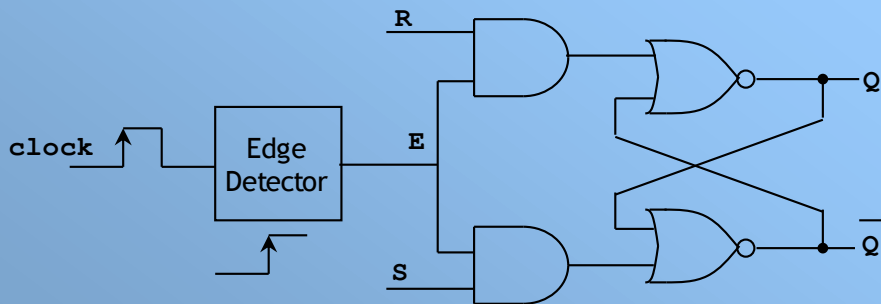Positive-edge triggered →  
Negative-edge triggered →



```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity ff_sr is  
  port ( s,r, clock: in std_logic;  
        q, qn: out std_logic);  
end ff_sr;
```

```
architecture bhv of ff_sr is  
  signal qt,qnt: std_logic;  
begin  
  process (s,r,clock)  
  begin
```

```
    if (clock'event and clock='1') then
```

```
      --if (clock'event and clock='0') then
```

```
        if s='1' and r='0' then  
          qt<='1'; qnt<='0';
```

```
        elsif s='0' and r='1' then  
          qt<='0'; qnt <='1';
```

```
        elsif s='1' and r='1' then  
          qt<='0'; qnt <= '0';
```

```
        end if;  
      end if;
```


```
    end process;
```

```
    q <= qt; qn <= qnt;
```

```
end bhv;
```

# ✓ SYNCHRONOUS PROCESSES


## ▪ D Flip Flop

 

clock	D	Q <sub>t+1</sub>
	0	0
	1	1

 
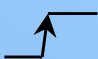
```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity ff_d is  
  port ( d, clock: in std_logic;  
        q, qn: out std_logic);  
end ff_d;
```


```
architecture bhv of ff_d is  
  signal qt, qnt: std_logic;  
begin  
  process (d, clock)  
  begin  
    if (clock'event and clock='1') then  
      qt<=d;  
    end if;  
  end process;  
  q <= qt; qn <= not(qt);  
end bhv;
```



# ✓ SYNCHRONOUS PROCESSES

## ▪ T Flip Flop

clock	T	$Q_{t+1}$
	0	$Q_t$
	1	$\overline{Q_t}$

 


```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity ff_t is  
  port ( t, clock: in std_logic;  
        q, qn: out std_logic);  
end ff_t;
```

```
architecture bhv of ff_t is  
  signal qt,qnt: std_logic;  
begin  
  process (t,clock)  
  begin  
    if (clock'event and clock='1') then  
      if t = '1' then  
        qt <= not(qt);  
      end if;  
    end if;  
  end process;  
  q <= qt; qn <= not(qt);  
end bhv;
```

# ✓ SYNCHRONOUS PROCESSES

## ▪ JK Flip Flop

 

clock	J	K	$Q_{t+1}$
	0	0	$Q_t$
	0	1	0
	1	0	1
	1	1	$\overline{Q_t}$

```
library ieee;
use ieee.std_logic_1164.all;

entity ff_jk is
  port ( s,r, clock: in std_logic;
        q, qn: out std_logic);
end ff_jk;

architecture bhv of ff_jk is
  signal qt,qnt: std_logic;
begin
  process (j,k,clock)
  begin
    if (clock'event and clock='1') then
      if j='1' and k='1' then
        qt<= not(qt);
      elsif j='1' and k='0' then
        qt<='0';
      elsif j='0' and k='1' then
        qt<='1';
      end if;
    end if;
  end process;
  q <= qt; qn <= qnt;
end bhv;
```


# ✓ SYNCHRONOUS PROCESSES

- D Flip Flop D with asynchronous inputs: 'clrn', 'prn'

- clrn = '0' → q = '0'
- prn = '0' → q = '1'

- These inputs force the outputs to a value immediately.

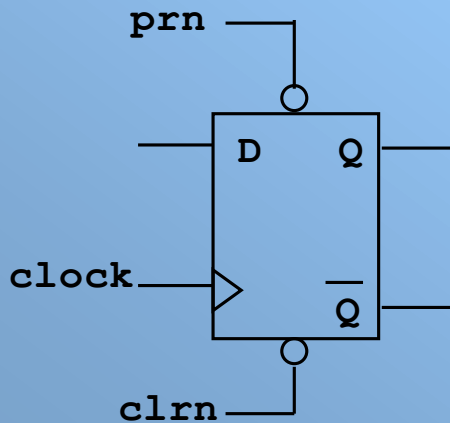- This is a useful feature if we want to initialize the circuit with no regards to the rising (or falling) clock edge



```
library ieee;
use ieee.std_logic_1164.all;


entity ff_dp is
  port ( d,clrn,prn,clock: in std_logic;
        q, qn: out std_logic);
end ff_dp;
```

```
architecture bhv of ff_dp is
  signal qt,qnt: std_logic;
begin
  process (d,clrn,prn,clock)
  begin
    if clrn = '0' then
      qt <= '0';
    elsif prn = '0' then
      qt <= '1';
    elsif (clock'event and clock='1') then
      qt <= d;
    end if;
  end process;
  q <= qt; qn <= not(qt);
end bhv;
```

# ✓ SYNCHRONOUS PROCESSES

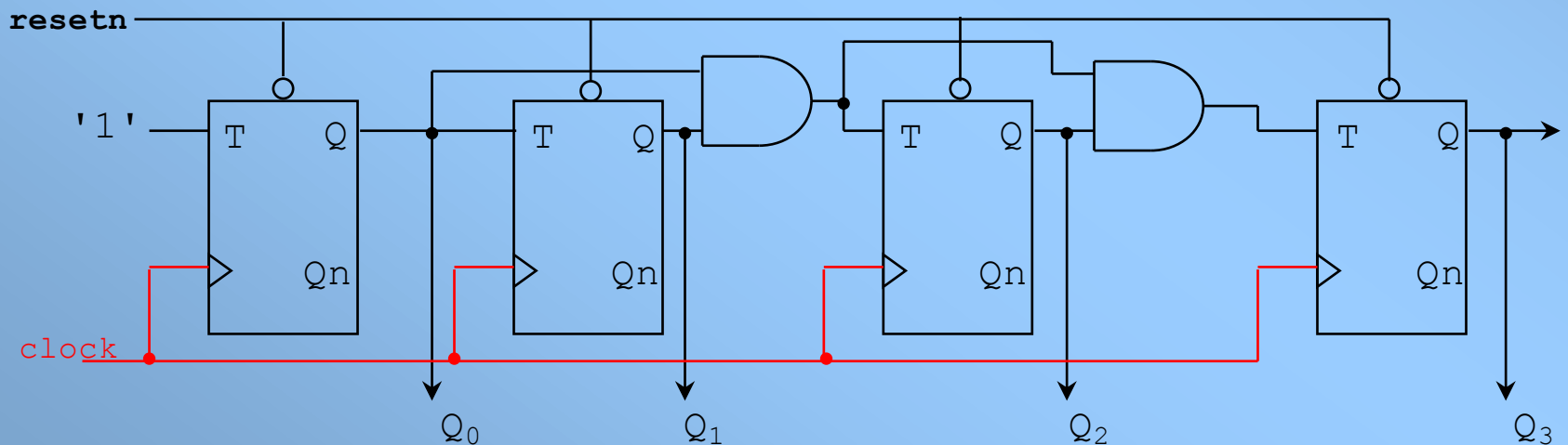
## ▪ Synchronous Counters

- Counters are very useful in digital systems. They can count the number of occurrences of a certain event, generate time intervals for task control, track elapsed time between two events, etc.
- Synchronous counters change their output on the clock edge (rising or falling). Counters are made of flip flops and combinatorial logic. Every flip flop in a synchronous counter shares the same clock signal. The figure shows a 4-bit synchronous counter (0000 to 1111). A 'resetrn' signal is also included to initialize the count.


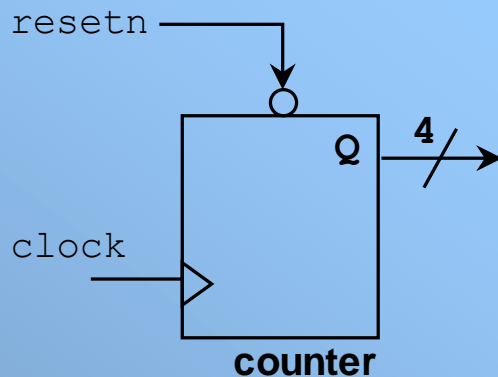
# ✓ 4-bit Synchronous counter with asynchronous active-low reset

- The 'resetn' signal sets the output to "0000" disregarding the clock edge



```
library ieee;
use ieee.std_logic_1164.all;


entity my_count4b is
  port ( clock, resetn: in std_logic;
        Q: out integer range 0 to 15);
end my_count4b;

architecture bhv of my_count4b is
  signal Qt: integer range 0 to 15;
begin
  process (resetn,clock)
  begin
    if resetn = '0' then
      Qt <= 0;
    elsif (clock'event and clock='1') then
      Qt <= Qt + 1;
    end if;
  end process;
  Q <= Qt;
end bhv;
```


 
# ✓ 4-bit Synchronous counter with asynchronous active-low reset and enable

- Note that the enable signal 'E' is synchronous, thus it is only considered on the rising clock edge




```
library ieee;
use ieee.std_logic_1164.all;

entity my_count4b_E is
    port ( clock, resetn, E: in std_logic;
          Q: out integer range 0 to 15);
end my_count4b_E;

architecture bhv of my_count4b_E is
    signal Qt: integer range 0 to 15;
begin
    process (resetn,clock, E)
    begin
        if resetn = '0' then
            Qt <= 0;
        elsif (clock'event and clock='1') then
            if E = '1' then
                Qt <= Qt + 1;
            end if;
        end if;
    end process;
    Q <= Qt;
end bhv;
```

# ✓ 4-bit Synchronous BCD counter with asynchronous active-low reset

- It counts from 0000 to 1001

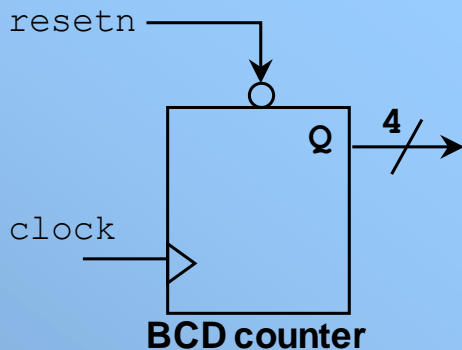


```
library ieee;
use ieee.std_logic_1164.all;

entity my_bcd_count is
    port ( clock, resetn: in std_logic;
          Q: out integer range 0 to 15);
end my_bcd_count;

architecture bhv of my_bcd_count is
    signal Qt: integer range 0 to 15;
begin
    process (resetn,clock)
    begin
        if resetn = '0' then
            Qt <= 0;
        elsif (clock'event and clock='1') then
            if Qt = 9 then
                Qt <= 0;
            else
                Qt <= Qt + 1;
            end if;
        end if;
    end process;
    Q <= Qt;
end bhv;
```
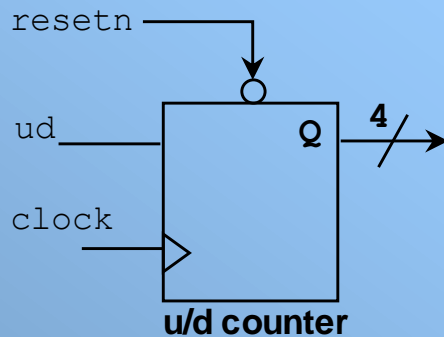
# ✓ 4-bit Synchronous up/down counter with asynchronous active-low reset

- $ud = 0 \rightarrow$  down
- $ud = 1 \rightarrow$  up
- When  $Q_t = 0000$ , then  $Q_t \leq Q_{t-1}$  will result in  $Q_t = 1111$




```
library ieee;
use ieee.std_logic_1164.all;

entity my_ud_count is
    port ( clock, resetn, ud: in std_logic;
          Q: out integer range 0 to 15);
end my_ud_count;

architecture bhv of my_ud_count is
    signal Qt: integer range 0 to 15;
begin
    process (resetn, clock, ud)
    begin
        if resetn = '0' then
            Qt <= 0;
        elsif (clock'event and clock='1') then
            if ud = '0' then
                Qt <= Qt - 1;
            else
                Qt <= Qt + 1;
            end if;
        end if;
    end process;
    Q <= Qt;
end bhv;
```

# ✓ 4-bit Synchronous counter with parallel load

- Here, we use Q as vector.

 

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

entity my_lcount is
  port ( clock, resetn,load: in std_logic;
        data: in std_logic_vector(3 downto 0);
        Q: out std_logic_vector(3 downto 0));
end my_lcount;
```


```
architecture bhv of my_lcount is
  signal Qt: std_logic_vector(3 downto 0);
begin
  process (resetn,clock,load)
  begin
    if resetn = '0' then
      Qt <= "0000";
    elsif (clock'event and clock='1') then
      if load = '1' then
        Qt <= data;
      else
        Qt <= Qt + "0001";
      end if;
    end if;
  end process;
  Q <= Qt;
end bhv;
```

# ✓ *SYNCHRONOUS PROCESSES*

- **Registers**
- These are sequential circuits that store the values of signals. There exist many register types: registers to handle interruptions in a PC, microprocessor registers, etc.
- A register that can hold 'n' bits is a collection of 'n' D-type flip flops
- Register types:
  - Simple Register (with/without enable)
  - Parallel access shift register (parallel output/serial output0.
  - Shift register (with/without enable)
    - Serial input, parallel output
    - Serial input, serial outputl
 
# ✓ PARALLEL LOAD, PARALLEL OUTPUT

- 8-bit register with enable and asynchronous reset




```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity reg8 is  
    port (clock, resetn, E: in std_logic;  
          D: in std_logic_vector (7 downto 0);  
          Q: out std_logic_vector (7 downto 0));  
end reg8;
```

```
architecture bhv of reg8 is  
begin  
    process (resetn,E,clock)  
    begin  
        if resetn = '0' then  
            Q <= (others => '0');  
        elsif (clock'event and clock = '1') then  
            if E = '1' then  
                Q <= D;  
            end if;  
        end if;  
    end process;  
end bhv;
```


# ✓ REGISTER: Serial Input, Serial/Parallel Output

- Shifting to the right.

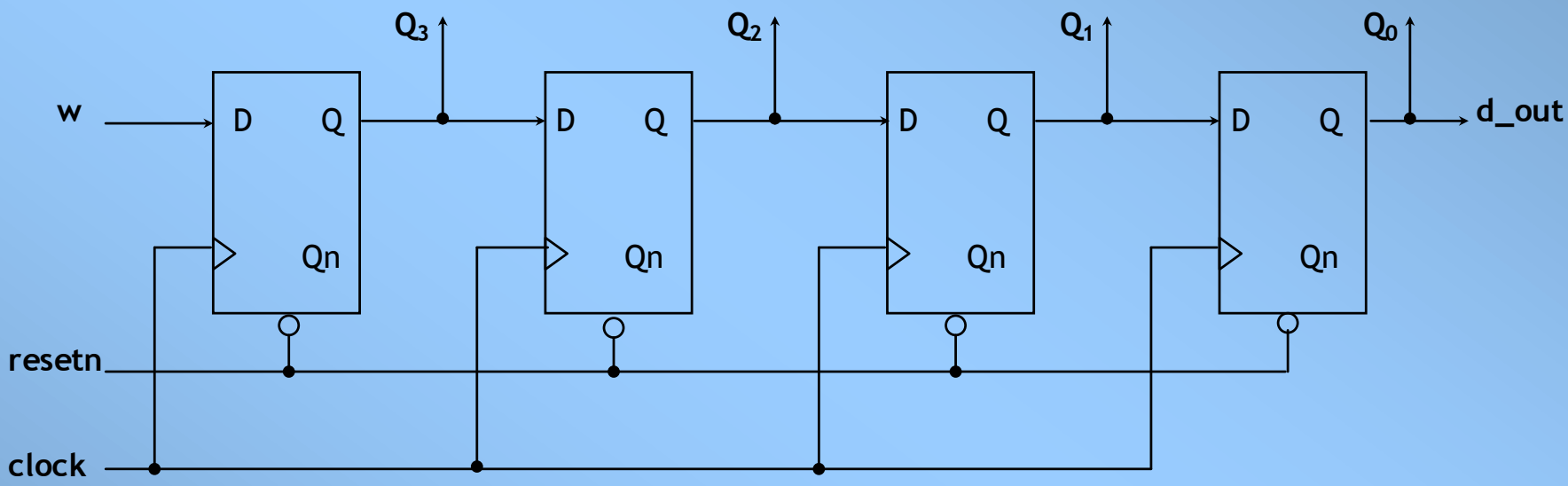
 
# ✓ REGISTER

- 4-bit register:
  - Parallel/serial load
  - Parallel/serial output
  - Shifting to the right
- The signal 'L' decides whether the load is parallel or serial
- 'Dout': serial output
- 'Q': parallel output



```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity reg_t is  
    port (clock, resetn, L,w: in std_logic;  
          Dout: out std_logic;  
          D: in std_logic_vector (3 downto 0);  
          Q: out std_logic_vector (3 downto 0));  
end reg_t;  
  
architecture bhv of reg_t is  
begin  
    process (resetn,L,clock)  
    begin  
        if resetn = '0' then  
            Q <= "0000";  
        elsif (clock'event and clock = '1') then  
            if L = '1' then  
                Q <= D;  
            else  
                Q(0) <= Q(1); Q(1) <= Q(2);  
                Q(2) <= Q(3); Q(3) <= w;  
            end if;  
        end if;  
    end process;  
    Dout <= Q(0);  
end bhv;
```



# ✓ REGISTER

- Alternative VHDL code:

- 4-bit register:

Parallel/serial load


Parallel/serial output

Shifting to the right

- The signal 'L' decides whether the load is parallel or serial

- 'Dout': serial output

- 'Q': parallel output

 


```
library ieee;
use ieee.std_logic_1164.all;

entity reg_t is
    port (clock, resetn, L,w: in std_logic;
          Dout: out std_logic;
          D: in std_logic_vector (3 downto 0);
          Q: out std_logic_vector (3 downto 0));
end reg_t;

architecture bhv of reg_t is
begin
    process (resetn,L,clock)
    begin
        if resetn = '0' then
            Q <= "0000";
        elsif (clock'event and clock = '1') then
            if L = '1' then
                Q <= D;
            else
                gg: for i in 0 to 2 loop
                    Q(i) <= Q(i+1);
                end loop;
                Q(3) <= w;
            end if;
        end if;
    end process;
    Dout <= Q(0);
end bhv;
```
 
# ✓ REGISTER

- 4-bit register:
  - Parallel/serial load
  - Parallel/serial output
  - Shifting to the left
- The signal 'L' decides whether the load is parallel or serial
- 'Dout': serial output
- 'Q': parallel output



```
library ieee;
use ieee.std_logic_1164.all;

entity reg_i is
    port (clock, resetn, L,w: in std_logic;
          Dout: out std_logic;
          D: in std_logic_vector (3 downto 0);
          Q: out std_logic_vector (3 downto 0));
end reg_i;

architecture bhv of reg_i is
begin
    process (resetn,L,clock)
    begin
        if resetn = '0' then
            Q <= "0000";
        elsif (clock'event and clock = '1') then
            if L = '1' then
                Q <= D;
            else
                Q(3) <= Q(2); Q(2) <= Q(1);
                Q(1) <= Q(0); Q(0) <= w;
            end if;
        end if;
    end process;
    Dout <= Q(3);
end bhv;
```

# ✓ REGISTER

- Alternative VHDL code:

- 4-bit register:

Parallel/serial load


Parallel/serial output

Shifting to the left

- The signal 'L' decides whether the load is parallel or serial

- 'Dout': serial output

- 'Q': parallel output

 

```
library ieee;
use ieee.std_logic_1164.all;

entity reg_i is
port (clock, resetn, L,w: in std_logic;
      Dout: out std_logic;
      D: in std_logic_vector (3 downto 0);
      Q: out std_logic_vector (3 downto 0));
end reg_i;

architecture bhv of reg_i is
begin
process (resetn,L,clock)
begin
if resetn = '0' then
Q <= "0000";
elsif (clock'event and clock = '1') then
if L = '1' then
Q <= D;
else
gg: for i in 1 to 3 loop
Q(i) <= Q(i-1);
end loop;
Q(0) <= w;
end if;
end if;
end process;
Dout <= Q(3);
end bhv;
```